

Session 2: Analog Circuits

Lab

Power / Energy

Series / Parallel

Small Signal

Applications

1

Outline

1. Lab	████
2. Power	████
3. Ser/Parl	████████
4. Small sig.	████████
5. Applic	████████

- ⊙ Lab hits
 - Power Supply, Oscilloscope , Breadboard , Multimeters
- ⊙ Energy
 - Power an Energy for R, L, C
- ⊙ Series / Parallel
 - LTI & NLTI
 - Duality
 - 1-port 2-port Networks
 - Piecewise linear
- ⊙ Small Signal
 - Bias point, small signal model
 - Diode example
- ⊙ Applications
 - Rectifier, Voltage limiter
 - Zener

2

001

Lab

3

Power Supply

1. Lab	████
2. Power	████
3. Ser/Parl	████████
4. Small sig.	████████
5. Applic	████████

4

Breadboard

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

Vcc
GND

5

Oscilloscope

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

Trigger: ?

?

6

Oscilloscope Probe

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

Do not use oscilloscope probe
for power cables!

7

Digital Multimeters

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

8

Energy and Power

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

Voltage definition: $V \equiv \frac{W}{Q}$

$$V = \frac{\delta W}{\delta Q} = \frac{\delta W / \delta t}{\delta Q / \delta t} = \frac{P}{I} \rightarrow P = VI$$

Power in electrical eng! $p(t) = v(t)i(t)$

$$[J] \leftarrow W(t_0, t_1) \equiv \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} v(t)i(t) dt$$

$$\begin{cases} v_1 = v_2 \\ i_1 = -i_2 \end{cases} \rightarrow p_1 = -p_2 \quad \sum p = 0$$

9

Passivity

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

Resistance

Definition:

- Passive: always in I, II ($\forall p(t) \geq 0$) receives power ; consumes power
- Active: not passive a point in III or IV ($\exists p(t) < 0$) delivers power ; generate power

10

Energy stored in TI Capacitor

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

capacitance NLTI

$$q = \hat{q}(v) \quad i(t) = \frac{dq}{dt}$$

$$W(t_0, t_1) = \int_{t_0}^{t_1} v(t)i(t) dt = \int_{q(t_0)}^{q(t_1)} v(q) dq$$

Assume at $t = 0 : v = 0, q = 0$

$$\mathcal{E}_E(t) = \int_0^{q(t)} v(q) dq$$

If $q = Cv$

$$\mathcal{E}_E(t) = \frac{1}{2}Cv^2 = \frac{q^2}{2C}$$

Only for LTI Cap

11

Energy stored in TI Inductor

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

inductor NLTI

$$\varphi = \hat{\varphi}(i) \quad v(t) = \frac{d\varphi}{dt}$$

$$W(t_0, t_1) = \int_{t_0}^{t_1} v(t)i(t) dt = \int_{\varphi(t_0)}^{\varphi(t_1)} i(\varphi) d\varphi$$

Assume at $t = 0 : i = 0, \varphi = 0$ (no hysteresis)

$$\mathcal{E}_M(t) = \int_0^{\varphi(t)} i(\varphi) d\varphi$$

If $\varphi = Li$

$$\mathcal{E}_M(t) = \frac{1}{2}Li^2 = \frac{\varphi^2}{2L}$$

Only for LTI Inductor

12

4th Element, Memristor

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

13

Series / Parallel LTI

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

$$i = i_1 = i_2$$

$$v = v_1 + v_2 = (R_1 + R_2)i$$

$$R_{eq} = (R_1 + R_2)$$

$$i = \frac{v}{R_{eq}} = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2}$$

$$G_{eq} = G_1 + G_2$$

14

Series / Parallel NLTl

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

$$i = i_1 = i_2$$

$$v = \hat{R}_{eq}(i) = v_1 + v_2$$

$$= \hat{R}_1(i) + \hat{R}_2(i)$$

adding voltages at equal currents
true for current controlled

$$v = v_1 = v_2$$

$$i = \hat{G}_{eq}(v) = i_1 + i_2$$

$$= \hat{G}_1(v) + \hat{G}_2(v)$$

adding currents at equal voltages
true for voltage controlled

15

Series / Parallel NLTl

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

analysis

synthesis

Reverse the diode direction and fine $v - i$ curve

16

Piecewise Linear Approximation Technique – Synthesis

1. Lab	□□□□
2. Power	□□□□□
3. Ser/Parl	□□□□□□□
4. Small sig.	□□□□□□□□□□
5. Applic	□□□□□□□□

voltage controlled

current controlled

21

Piecewise Linear Approximation Technique – Synthesis

1. Lab	□□□□
2. Power	□□□□□
3. Ser/Parl	□□□□□□□
4. Small sig.	□□□□□□□□□□
5. Applic	□□□□□□□□

22

Quiescent Point

1. Lab	□□□□
2. Power	□□□□□
3. Ser/Parl	□□□□□□□
4. Small sig.	□□□□□□□□□□
5. Applic	□□□□□□□□

Small signal regime

$\tilde{v}_0 \ll V_0$
 $\tilde{i}_0 \ll I_0$

23

Quiescent (Bias) Point for NLTI

1. Lab	□□□□
2. Power	□□□□□
3. Ser/Parl	□□□□□□□
4. Small sig.	□□□□□□□□□□
5. Applic	□□□□□□□□

Linear 2-terminal network

Thevenin equivalent

$i_a = 4v_a^2$
 $v_a = v_b$
 $i_a = -i_b$

24

Small-Signal Analysis (for NLTI)

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

$v_s(t) = \tilde{v}_0 \sin \omega t$

Small-signal condition $\tilde{v}_0 \ll V_0$

$$i = \hat{i}(v) \quad \begin{cases} I_Q = \hat{i}(V_Q) \\ V_Q = V_0 - RI_Q \end{cases}$$

$$\begin{cases} v(t) \equiv V_Q + \tilde{v}(t) \\ i(t) \equiv I_Q + \tilde{i}(t) \end{cases}$$

$$I_Q + \tilde{i}(t) = \hat{i}(V_Q + \tilde{v}(t))$$

25

Small-Signal Analysis (for NLTI)

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

Taylor series:

$$f(x_0 + \delta x) \approx f(x_0) + \left. \frac{df}{dx} \right|_{x_0} (\delta x) + \frac{1}{2} \left. \frac{d^2 f}{dx^2} \right|_{x_0} (\delta x^2) + \dots$$

$v_s(t) = \tilde{v}_0 \sin \omega t$

Small-signal condition $\tilde{v}_0 \ll V_0$

$$i = \hat{i}(v) \quad \begin{cases} I_Q = \hat{i}(V_Q) \\ V_Q = V_0 - RI_Q \end{cases}$$

$$\begin{cases} v(t) \equiv V_Q + \tilde{v}(t) \\ i(t) \equiv I_Q + \tilde{i}(t) \end{cases}$$

$$I_Q + \tilde{i}(t) = \hat{i}(V_Q + \tilde{v}(t))$$

$$I_Q + \tilde{i}(t) \approx \hat{i}(V_Q) + \left. \frac{d\hat{i}}{dv} \right|_{V_Q} \tilde{v}(t)$$

dc $I_Q = \hat{i}(V_Q)$

ac $\tilde{i}(t) \approx \underbrace{\left. \frac{d\hat{i}}{dv} \right|_{V_Q}}_{G_{SS}} \tilde{v}(t)$

$G_{SS} = 1/R_{SS}$

R_{SS} small signal resistance

26

Small-Signal Analysis (for NLTI)

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

Step1: Find Bias Point!

Small-signal condition $\tilde{v}_0 \ll V_0$

$$\begin{cases} v(t) \equiv V_Q + \tilde{v}(t) \\ i(t) \equiv I_Q + \tilde{i}(t) \end{cases}$$

Step2: Small Signal Analysis!

$$\tilde{v}(t) = \frac{R_{SS}}{R + R_{SS}} v_s(t)$$

$v_s(t) = \tilde{v}_0 \sin \omega t$

$$R_{SS} = \left. \frac{1}{\frac{d\hat{i}}{dv}} \right|_{V_Q} = \left. \frac{dy}{dx} \right|_{I_Q}$$

27

Example - Diode

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

NLTI: Diode

$$i_D = I_S (e^{qv_D/nkT} - 1)$$

$$V_T = \left. \frac{kT}{q} \right|_{300^\circ K} = 26mV$$

Forward biased diode: $i_D = I_S (e^{qv_D/nkT} - 1) \approx I_S e^{qv_D/nkT} \frac{v_d}{nV_T}$

$$i_D \approx I_S e^{qv_D/nkT} \left(1 + \frac{v_d}{nV_T} + \frac{1}{2} \left(\frac{v_d}{nV_T} \right)^2 + \dots \right) \approx I_D + I_D \frac{v_d}{nV_T}$$

$\frac{v_d}{nV_T} \ll 1$

$r_d \equiv \frac{v_d}{i_d} = \frac{nV_T}{I_D}$ small signal resistance

$r_d = \left. \frac{1}{\frac{di}{dv}} \right|_{V_D} = \frac{nV_T}{I_D}$

28

Example – Diode

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

small signal resistance

$$r_d = \frac{nV_T}{I_D}$$

NLTI: Diode

$$i_D = I_S (e^{qv_D/nkT} - 1)$$

$$V_T = \frac{kT}{q} \Big|_{300^\circ\text{K}} = 26\text{mV}$$

? How to solve bias (large signal) $I_D = I_S (e^{V_D/nV_T} - 1)$

29

Diode – Large Signal

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

NLTI: Diode

$$i_D = I_S (e^{qv_D/nkT} - 1)$$

$$V_T = \frac{kT}{q} \Big|_{300^\circ\text{K}} = 26\text{mV}$$

? How to solve bias (large signal)

30

Diode – Large Signal

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

$i_D = I_S (e^{qv_D/nkT} - 1)$

? How we should bias a diode?

? How we should bias a diode?

31

Example – Diode – Large Signal

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic.

$i_D = I_S (e^{qv_D/nkT} - 1)$

$v_D = V_{DD} - i_D R$

Load line

$V_{DD} = 5\text{V}, R = 1\text{k}\Omega, I_S = 5 \times 10^{-14}\text{A}, V_T = 26\text{mV}$

iteration

- $v_D = 0 \rightarrow i_D = \frac{V_{DD} - v_D}{R} = 5\text{mA}$
- $v_D = V_T \ln\left(\frac{i_D}{I_S}\right) = 0.658 \rightarrow i_D = \frac{V_{DD} - v_D}{R} = 4.341\text{mA}$
- $v_D = V_T \ln\left(\frac{i_D}{I_S}\right) = 0.654864 \rightarrow i_D = \frac{V_{DD} - v_D}{R} = 4.345\text{mA}$
- $v_D = V_T \ln\left(\frac{i_D}{I_S}\right) = 0.654889 \rightarrow i_D = \dots$

32

Example - Diode - Large/Small Signal

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

$v_{in} = V_0 + \hat{v}_i \sin \omega t$

Bias: $V_{OUT} = V_0 - V_Y$ $I_D = \frac{V_0 - V_Y}{R}$

Small signal: $r_d = \frac{nV_T}{I_D}$ small signal resistance

$v_o = \frac{R}{R + r_d} \hat{v}_i \sin \omega t$

Final output: $v_{out} = (V_0 - V_Y) + \frac{R}{R + r_d} \hat{v}_i \sin \omega t$

33

Example - Diode - Large/Small Signal

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

$v_s = 1V + 0.1V \sin \omega t$; $V_Y = 0.7V$

DC / bias

$I_D = \frac{3 - 1 - 0.7}{100 + 120} = 6.36 \text{ mA}$

$r_d = \frac{V_T}{I_D} = 3.9 \Omega$

AC / small signal

$\hat{v}_o = \frac{r_d}{220 + r_d} 0.1 = 1.75 \text{ mV}$

$v_o = -0.7 + 1.75 \text{ mV} \sin \omega t$

34

Example 01

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

Find $v_{in} - v_{out}$ assume $V_Y = 0, 0.7V$

1: (F) If $i_D > 0$

$v_{out} = v_{in}$
 condition $i_D > 0$
 $\rightarrow i_D = v_{out}/R > 0 \rightarrow v_{out} > 0$
 $v_{in} > 0$

1: (R) If $v_D < 0$

$v_{out} = 0$ condition $v_D < 0$
 $\rightarrow v_{in} - v_{out} < 0 \rightarrow v_{in} < 0$

35

Example 01

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

Find $v_{in} - v_{out}$ assume $V_Y = 0, 0.7V$

1: (F) If $i_D > 0$

$v_{out} = v_{in}$
 condition $i_D > 0$
 $\rightarrow i_D = v_{out}/R > 0 \rightarrow v_{out} > 0$
 $v_{in} > 0$

1: (R) If $v_D < 0$

$v_{out} = 0$ condition $v_D < 0$
 $\rightarrow v_{in} - v_{out} < 0 \rightarrow v_{in} < 0$

36

Example 01

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

37

Example 01

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

38

Example 01

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic


39

Voltage Limiter

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

40

1: D1:OFF, D2:OFF

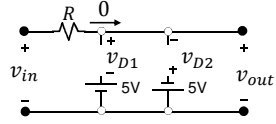

$$v_{D1} < 0 \rightarrow v_{out} - 5 < 0 \rightarrow v_{out} < 5$$

$$v_{D2} < 0 \rightarrow -v_{out} - 5 < 0 \rightarrow v_{out} > -5$$

condition $v_D < 0$
 $\rightarrow v_{in} - v_{out} < 0 \rightarrow v_{in} < 0$

Zener Diode – Voltage Regulator

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

large signal

Small signal

$$\delta v_o = \frac{r_z}{r_z + R} \delta v_i$$

45

Zener Diode – Voltage Regulator

1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

$R_{Lmin} < R_L < \infty$

$$I_Z < I_{max} \quad \frac{v_{URmax} - V_Z}{R} < I_{max}$$

$I_Z > I_{min}$

$$\frac{v_{URmin} - V_Z}{R} - \frac{V_Z}{R_{Lmin}} > I_{min}$$

46