

Session 4: Analog Circuits

BJT
Biasing
Single stage amplifier











Outline

1. Lab	
2. Power	
3. Ser/Parl	
4. Small sig.	
5. Applic	

◎ BJT Amplifier


BJT: Bipolar Junction Transistor

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

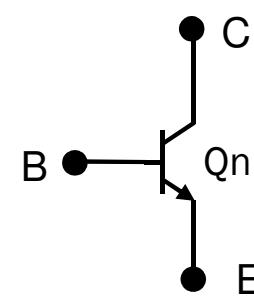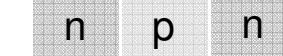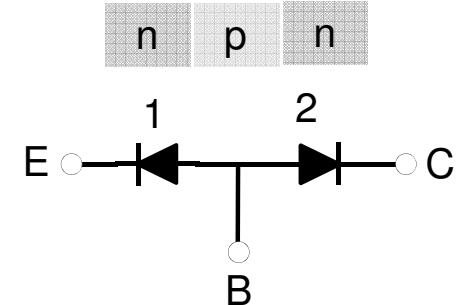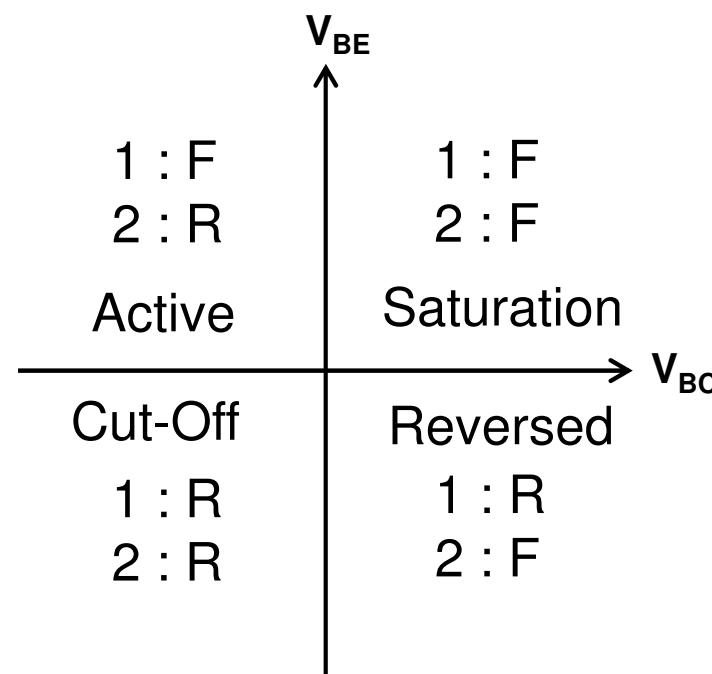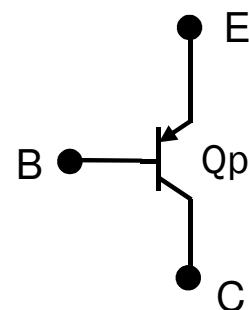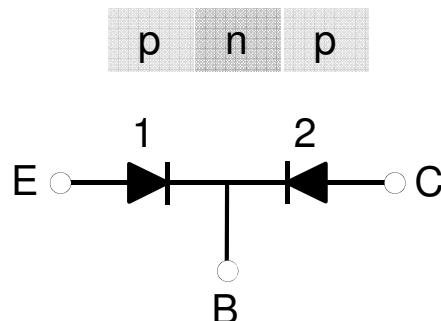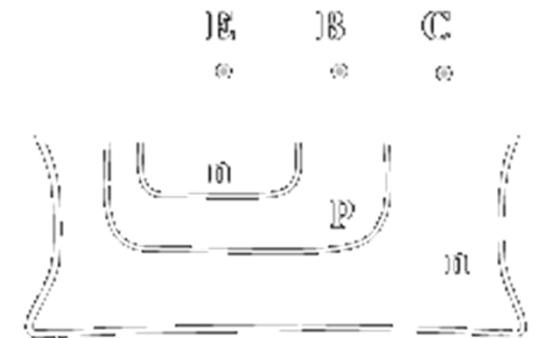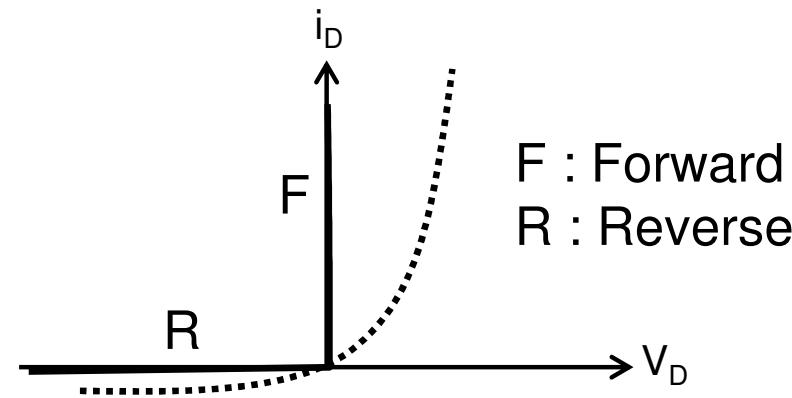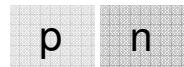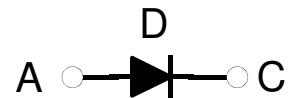


BJT: Bipolar Junction Transistor

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

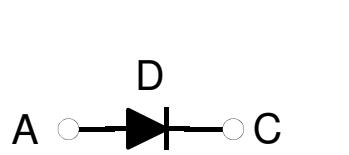



p n

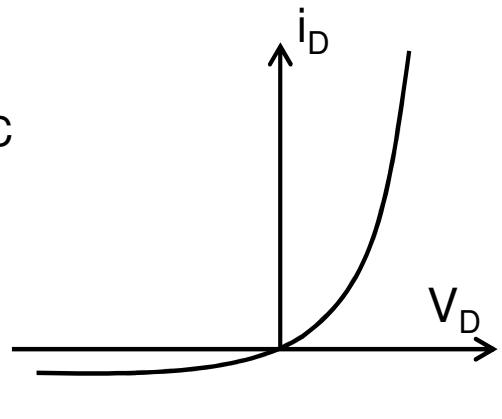

$$i_D \propto e^{v_D/nV_T}$$

$$\frac{\Delta v_D}{\Delta T} \approx -2 \frac{mV}{K} \Big|_{i_D=cte}$$
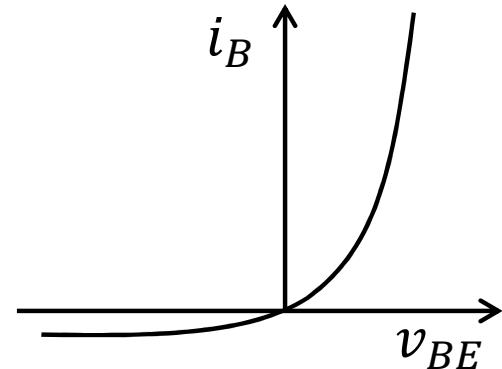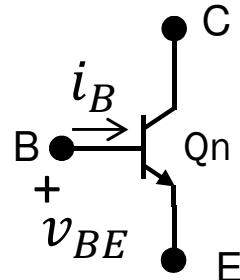
$$\frac{i_D(T_2)}{i_D(T_1)} \approx 2^{(T_2-T_1)/10K}$$



$$i_B \propto e^{v_{BE}/nV_T}$$


$$\frac{\Delta v_{BE}}{\Delta T} \approx -2 \frac{mV}{K} \Big|_{i_E=cte}$$

$$\frac{i_C(T_2)}{i_C(T_1)} \approx 2^{(T_2-T_1)/10K}$$


BJT Configurations

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |


CE: Common Emitter

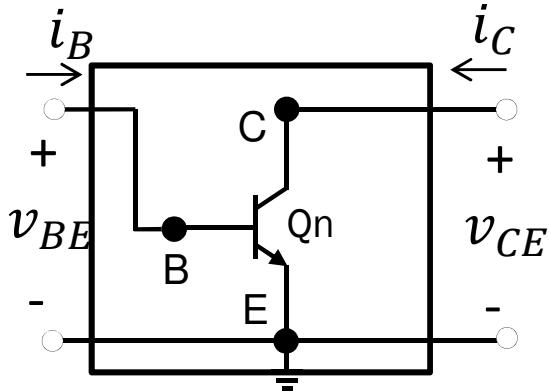

CB: Common Base

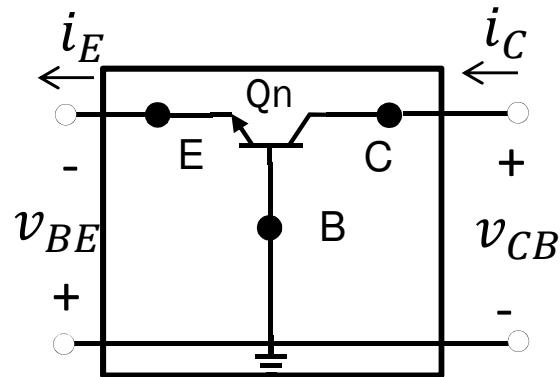

CC: Common Collector

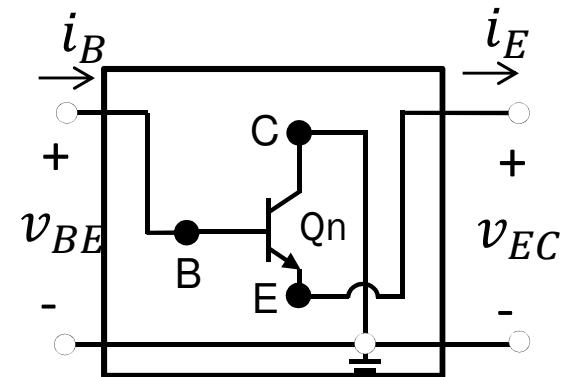

Input Characteristic

i_B vs. v_{BE} for different V_{CE}

Output Characteristic


i_C vs. v_{CE} for different V_{BE} or i_B

Transfer Characteristic


i_C vs. v_{BE} or i_B for different V_{CE}

CE: Common Emitter

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

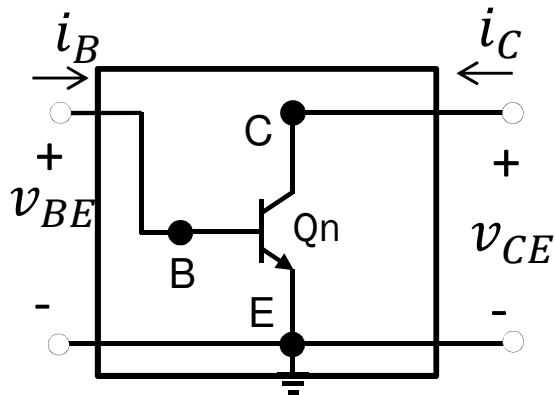


Input Characteristic

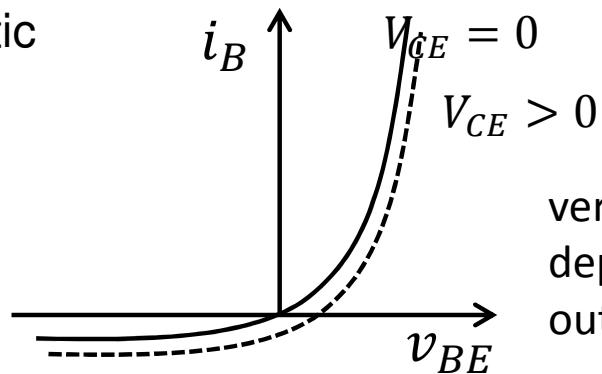

very little dependence to output voltage


Output Characteristic

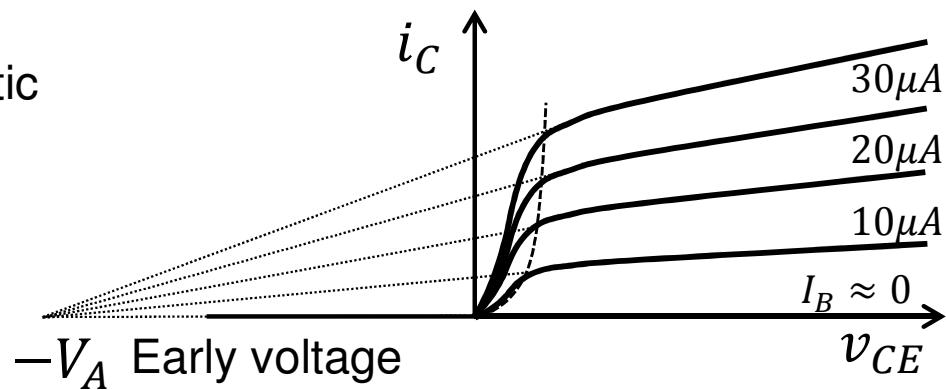

Active:

$$i_C = I_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A} \right)$$


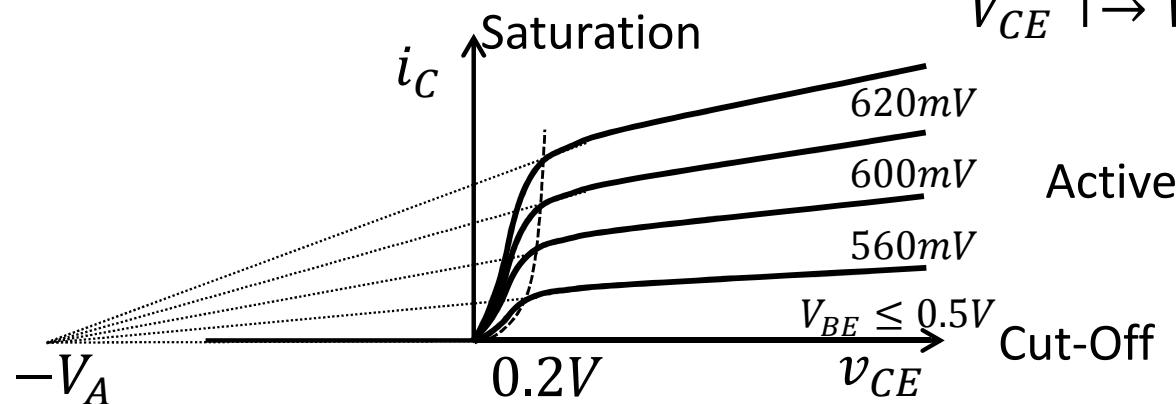
$V_{CE} \uparrow \rightarrow W \uparrow \rightarrow \beta \uparrow \rightarrow I_C \uparrow$




Active

CE: Transistor Model

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

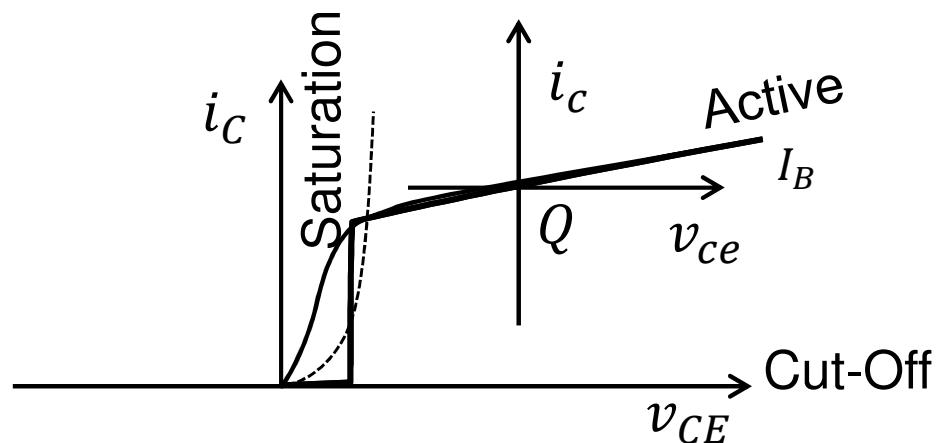
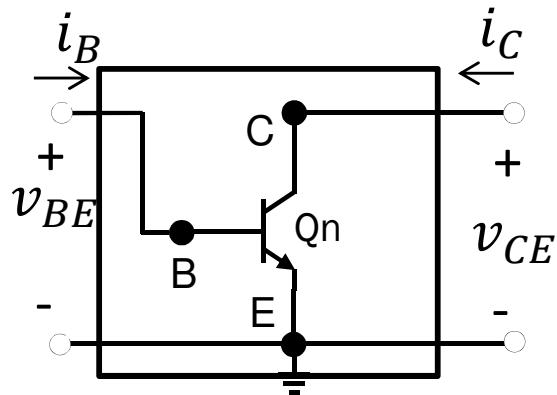


Output Characteristic

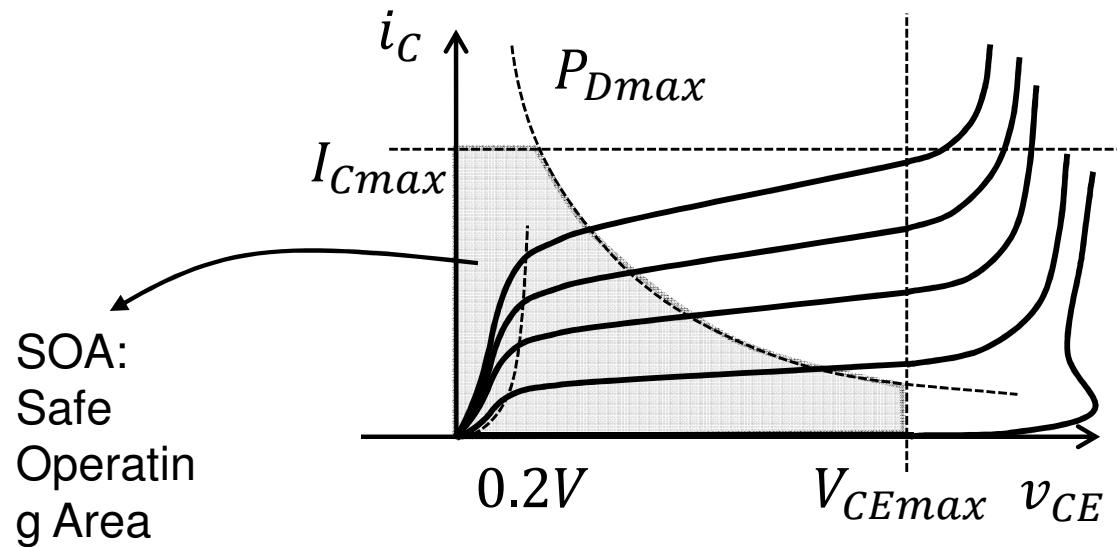

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

CE: Output Characteristic

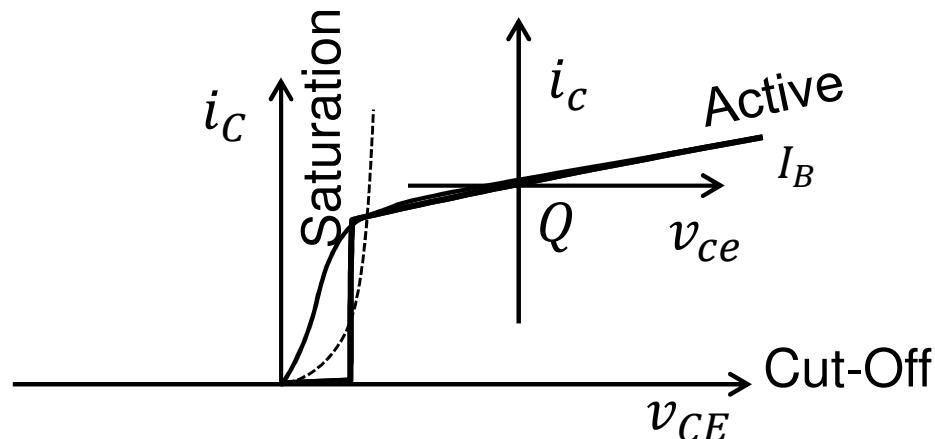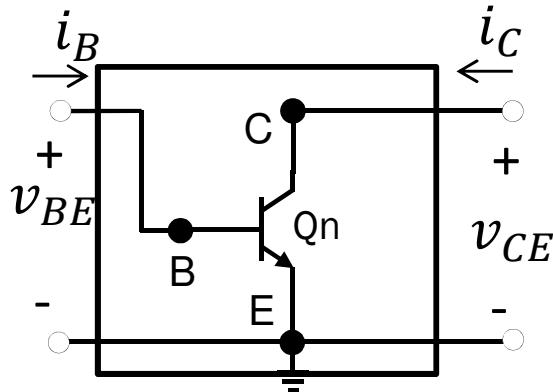

$$i_B = I'_S e^{\frac{v_{BE}}{nV_T}}$$

$$i_C \approx I_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right)$$

Ideally linear:

$$\beta = \frac{i_C}{i_B} = \frac{I_C}{I_B} = \frac{i_c}{i_b}$$

SPICE



$$BF = \beta_F = \left. \frac{i_C}{i_B} \right|_{V_{CB}=0}$$

$$BDC = \beta_{DC} = \left. \frac{i_C}{i_B} \right|_{I_C=I_Q} = \beta_F \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$BAC = \left. \frac{\partial i_C}{\partial i_B} \right|_{I_C=I_Q} = \frac{i_c}{i_b}$$


- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

Beta : Current Gain

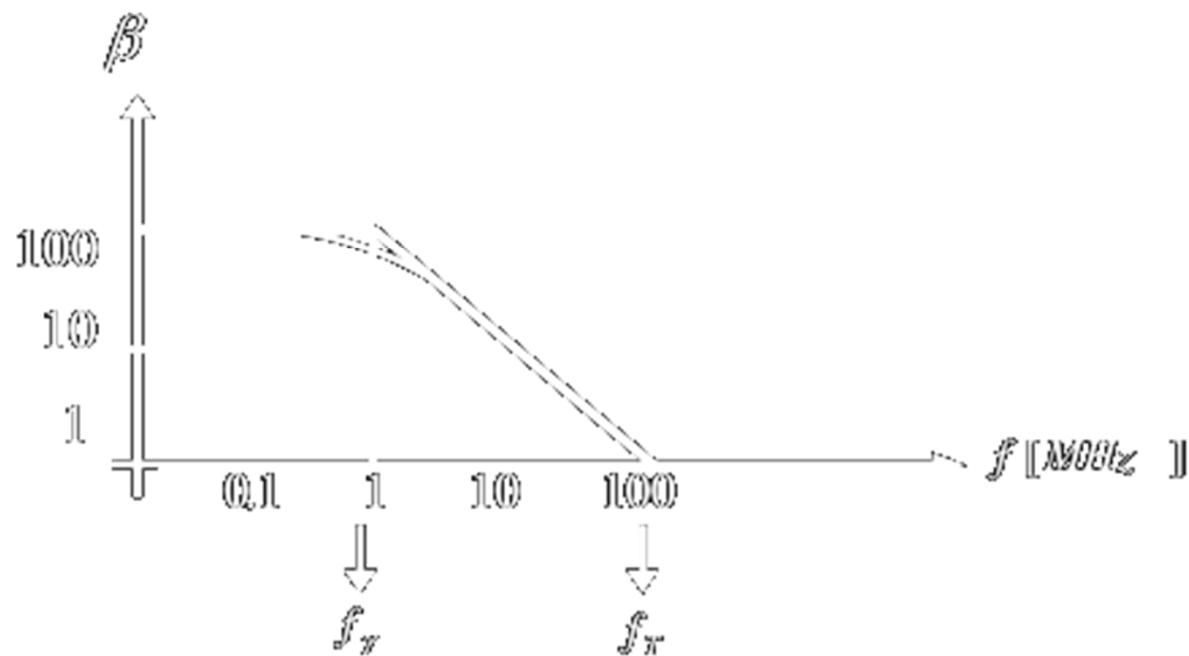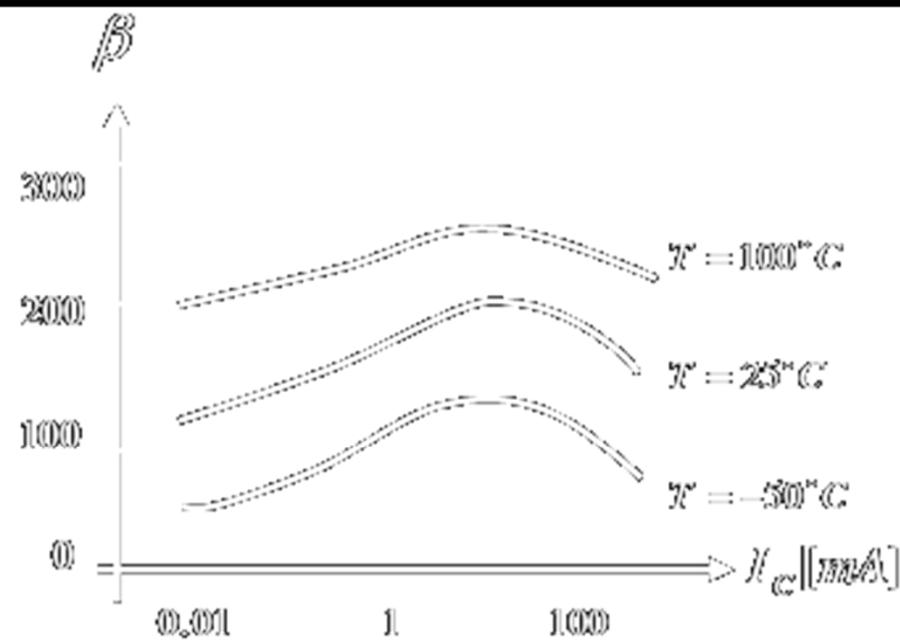


1. Lab
 2. Power
 3. Ser/Parl
 4. Small sig.
 5. Applic

CB: Common Base

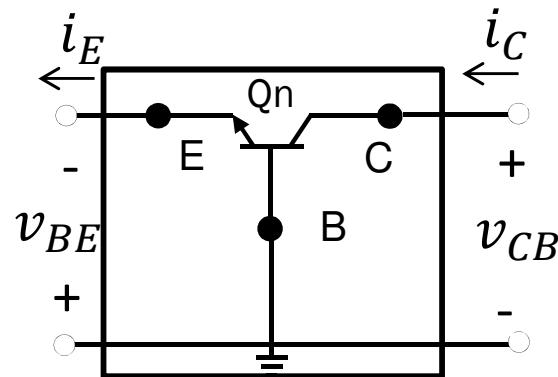


Output Characteristic

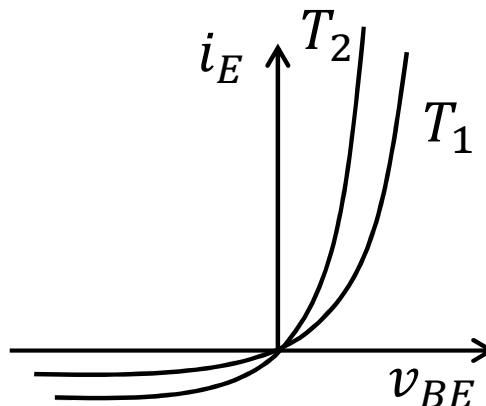


$$T_2 > T_1$$

$$\frac{\Delta v_{BE}}{\Delta T} \approx -2 \frac{mV}{K} \Big|_{i_E=cte}$$

Input Characteristic

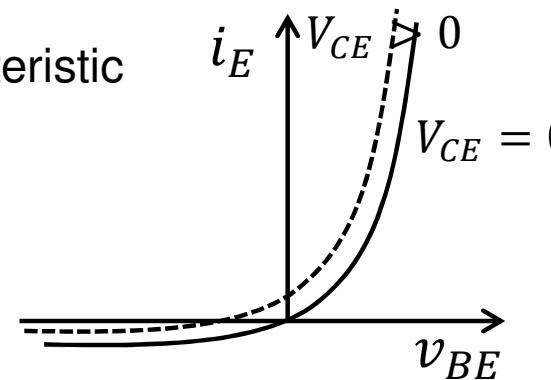

very little
dependence to
output voltage

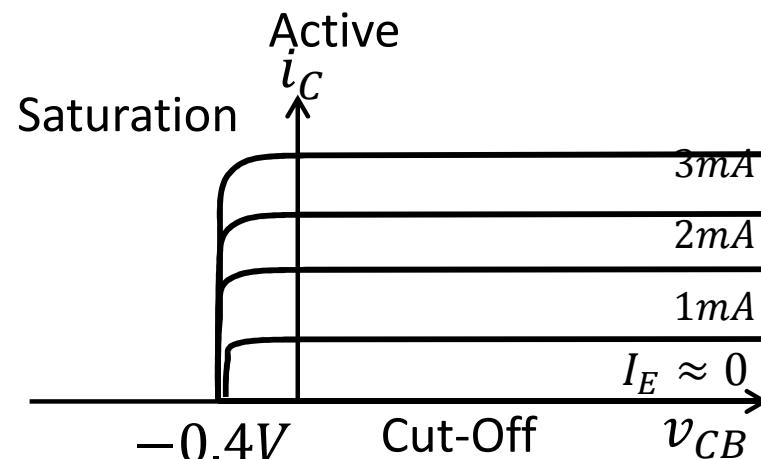








Active:

$$i_C = \alpha i_E$$

$$\alpha = \frac{\beta}{\beta + 1}$$



Large Signal Model

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

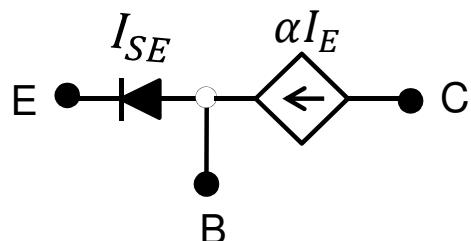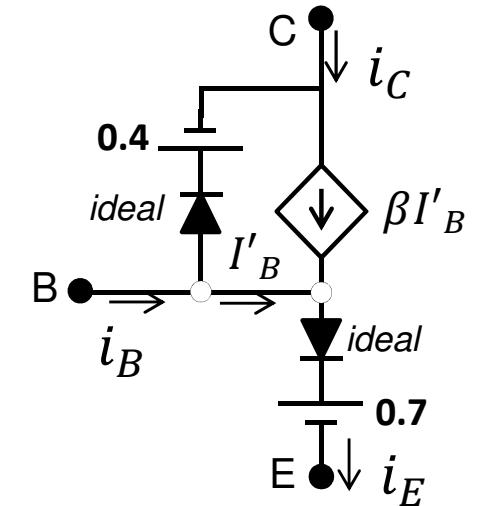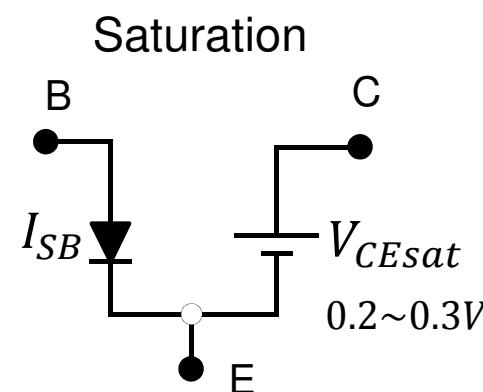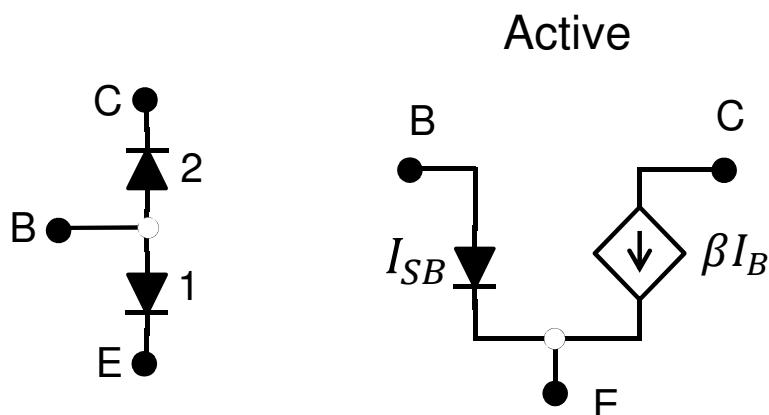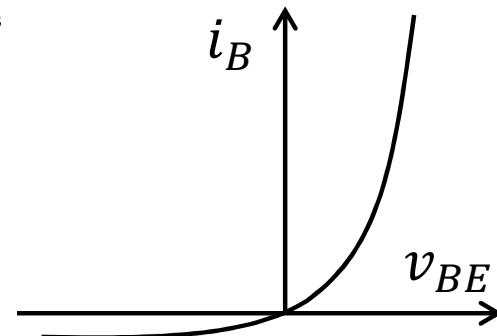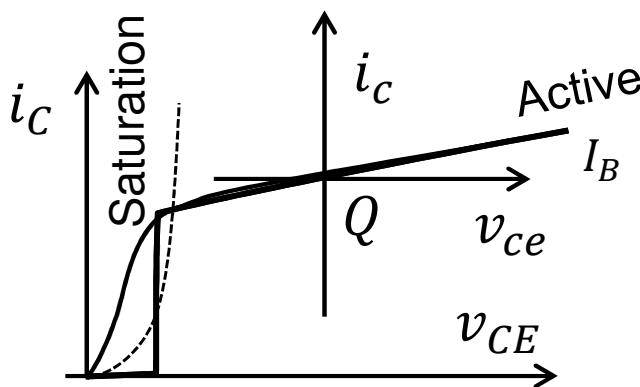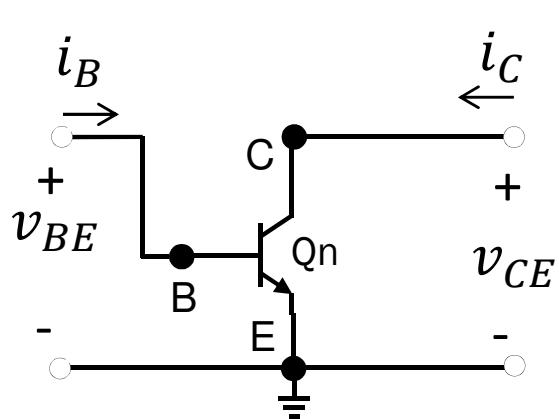



- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

Voltage Amplifier

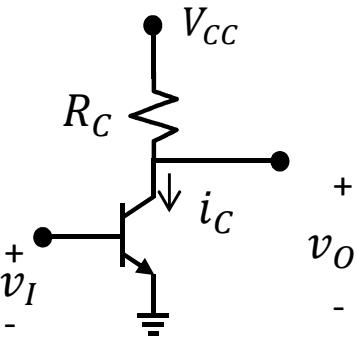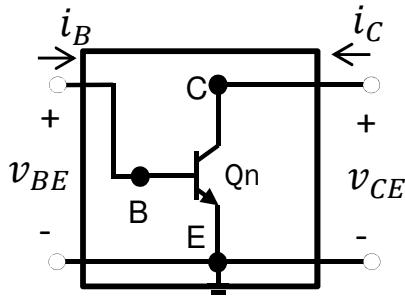





$$v_O = V_{CC} - R_C i_C$$
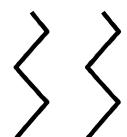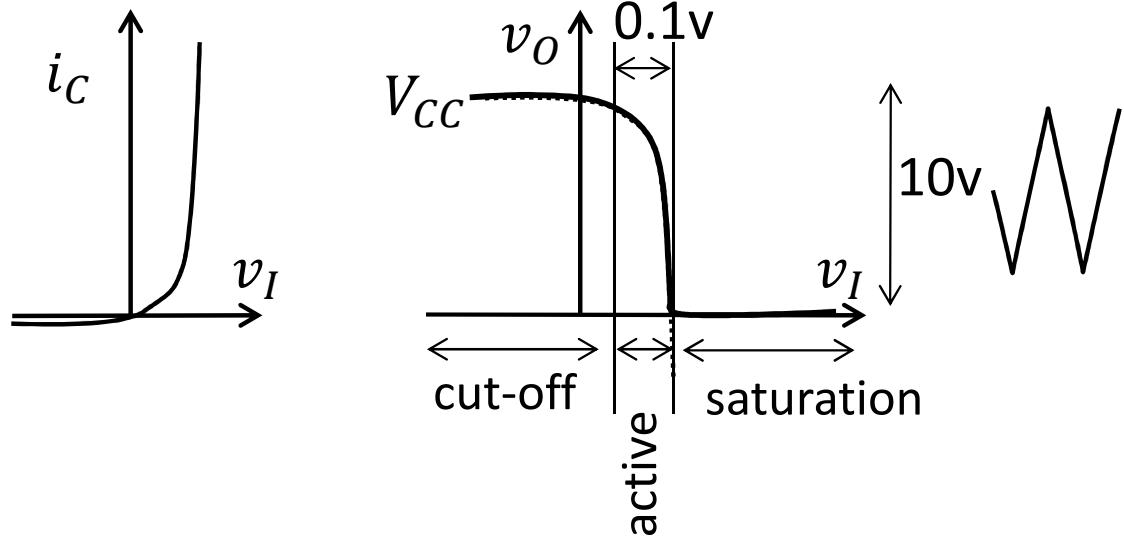
$$i_C = \beta i_B = I_S (e^{\frac{v_I}{V_T}} - 1)$$




- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

Biasing: $V_{BE} = \text{cte}$

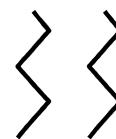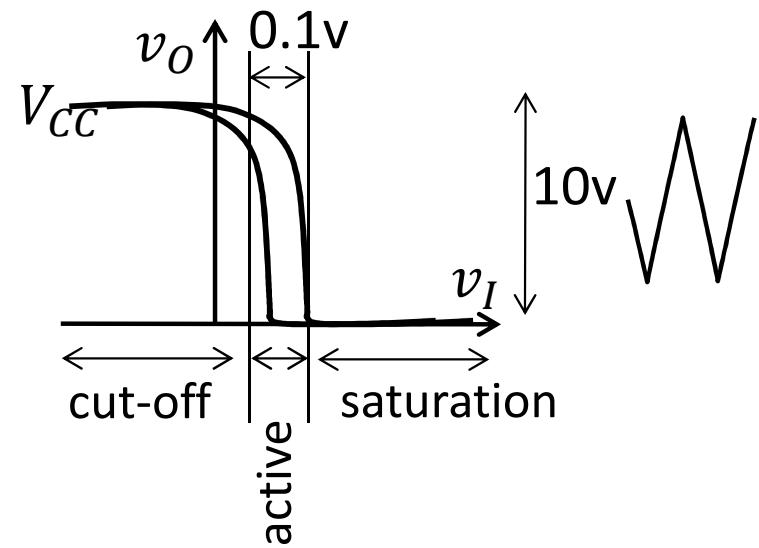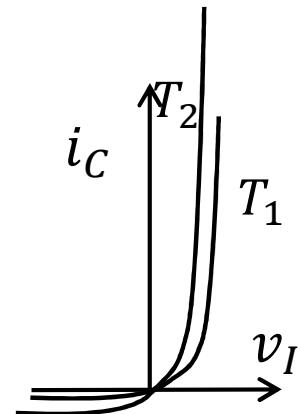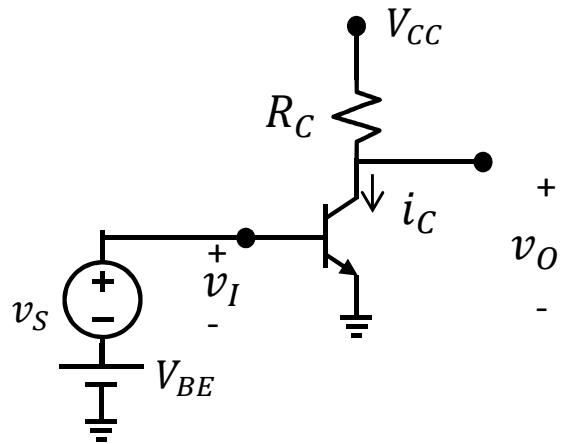

1. Lab	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
2. Power	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
3. Ser/Parl	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
4. Small sig.	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
5. Applic	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>

Biasing: $I_B = \text{cte}$

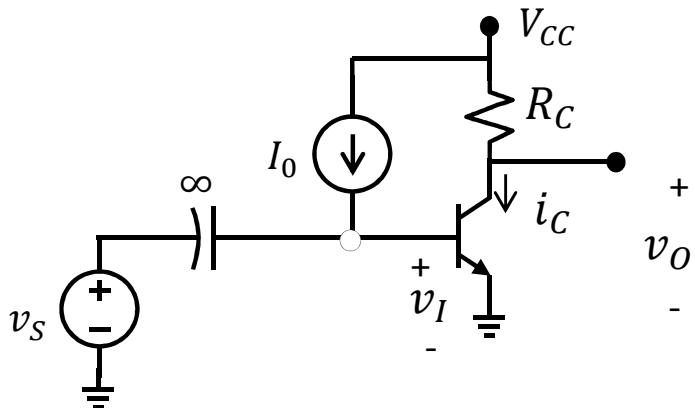

$$I_B = I_0$$

$$I_C = \beta I_B$$

$$V_{CC} = 10V$$

$$I_C = 1mA \quad \beta = 100$$


$$I_0 = 10\mu A$$

For max swing:

$$V_C \sim 5V \rightarrow R_C \sim 5k\Omega$$

For max gain:
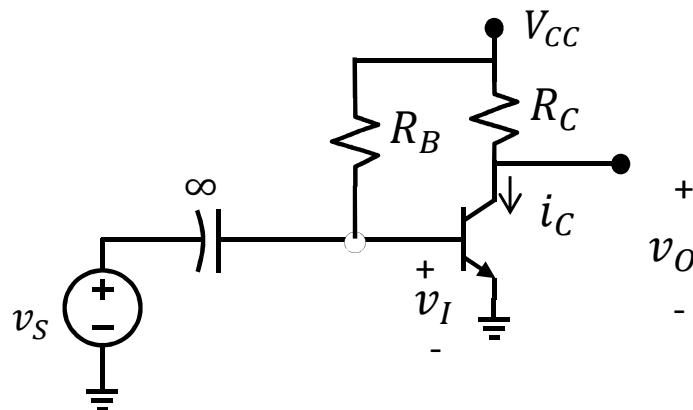
$$V_C \sim 0.3V \rightarrow R_C \sim 9.7k\Omega$$



$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$V_{CC} = 10V$$


$$I_C = 1mA \rightarrow R_B = 930k\Omega$$

What is the problem?

Replace it with transistor with $\beta = 250$


$$I_C = 2.5mA$$
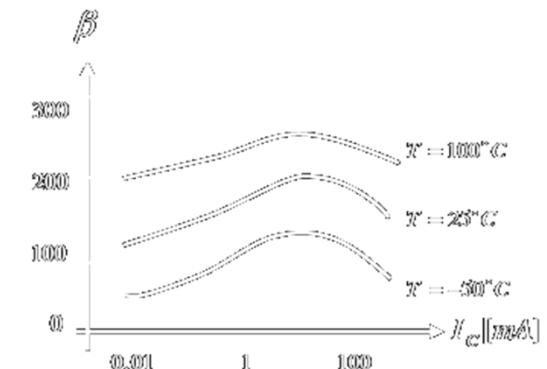
$$V_{CE} = 10 - 5 \times 2.5 = -2.5 < V_{CESat}$$



- | | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

Biasing: $I_B = \text{cte}$

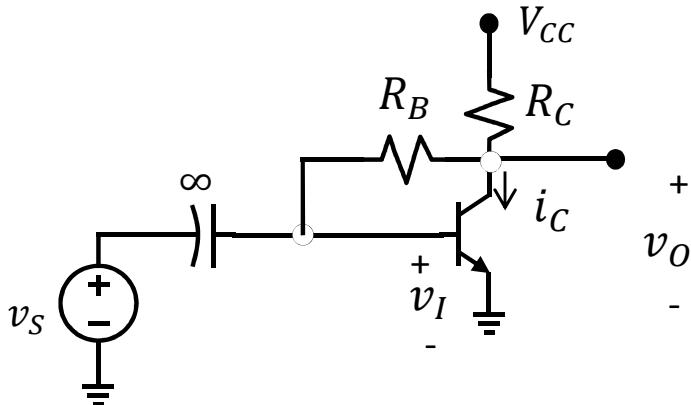


$$V_{CC} = 10V \quad I_C = 1mA \quad \beta = 100$$

For max swing: $V_C \sim 5V$



$$R_B = \frac{V_C - V_{BE}}{I_B} = \beta \frac{V_C - V_{BE}}{I_C}$$

$$\rightarrow R_B = 430k\Omega$$

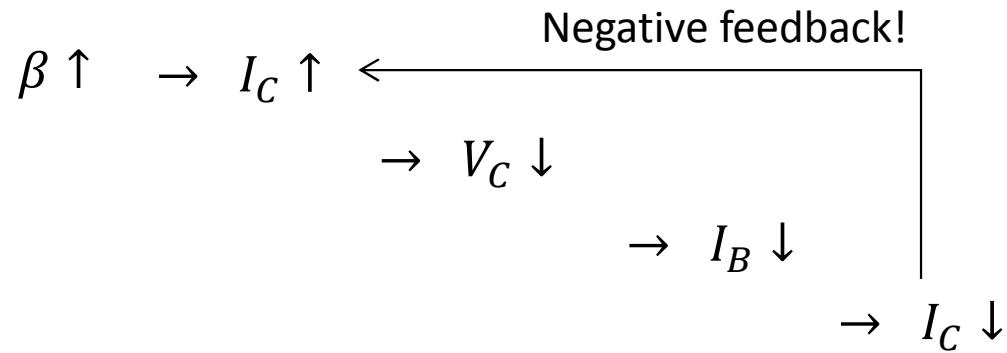

Biasing: $I_E = \text{cte}$

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

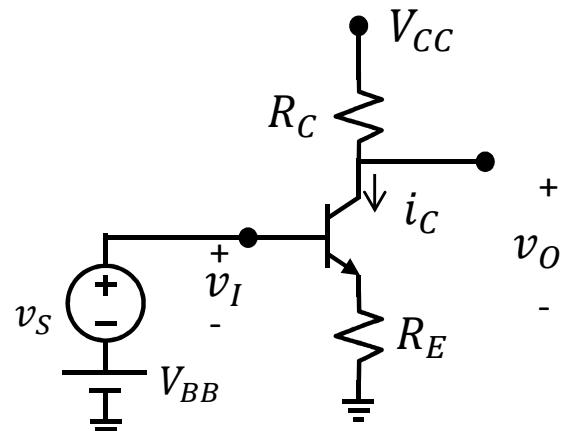
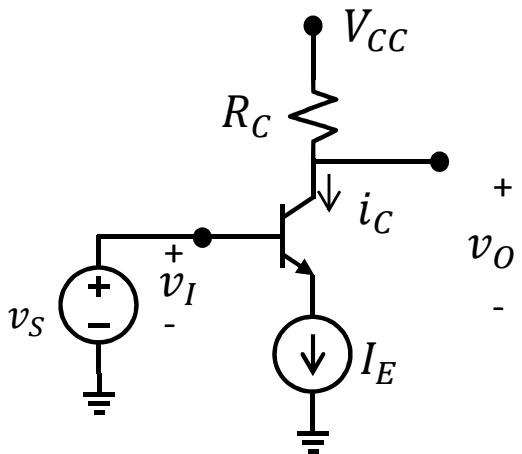


$$I_E = \frac{V_{BB} - V_{BE}}{R_E}$$


I_E independent of V_{BE}

$V_{BB} \gg V_{BE}$

$V_{BB} \sim 2.7V$

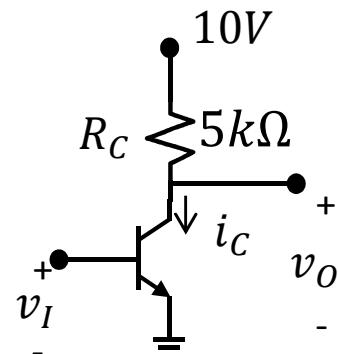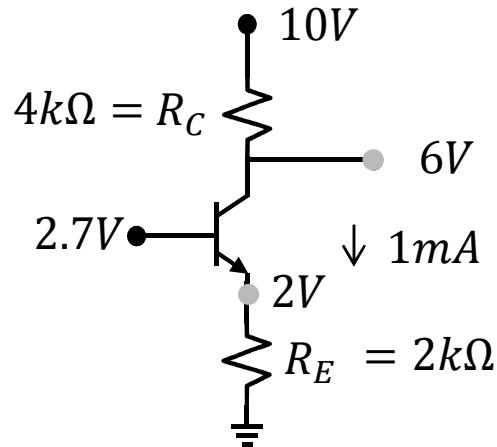


Where is the trade-off?

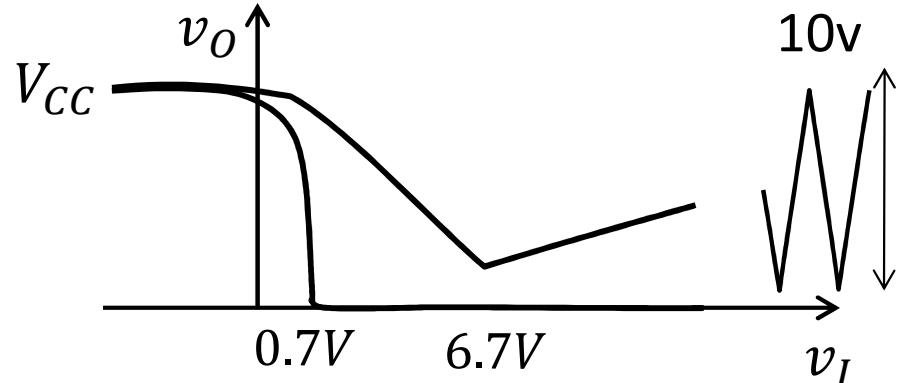

Biasing: $I_E = \text{cte}$



- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

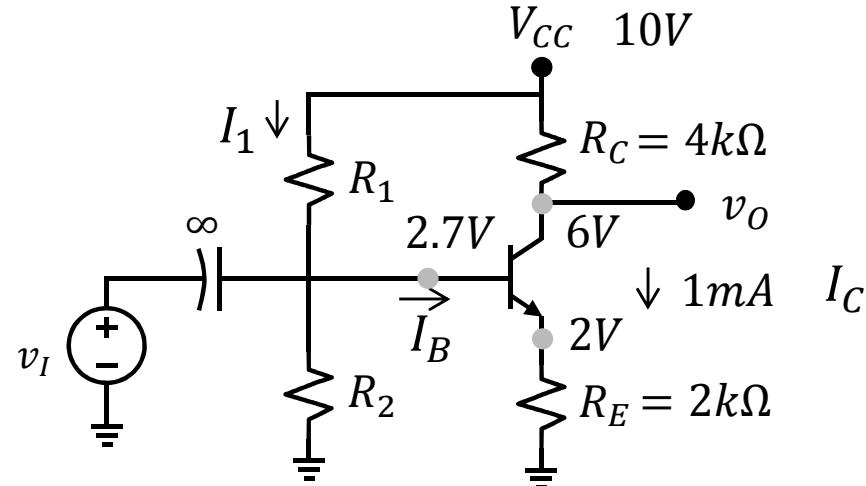

$$I_B = \frac{I_C}{\beta}$$

Assume: $I_1 \gg I_B$

$$V_B = \frac{R_2}{R_2 + R_1} V_{CC}$$

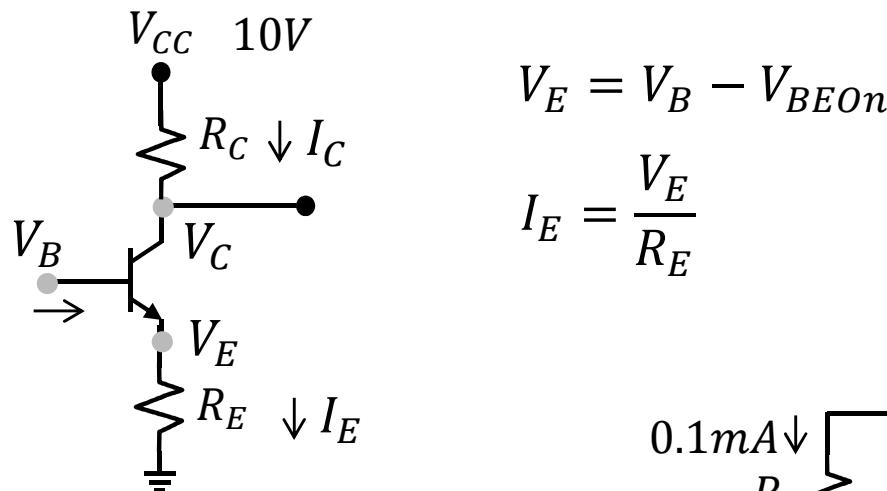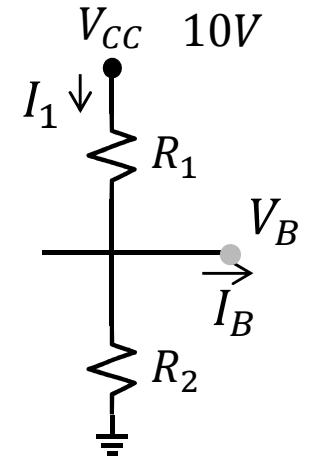


$$V_E = V_B - V_{BEon}$$

$$I_E = \frac{V_E}{R_E}$$

$$I_C = \alpha I_E \approx I_E$$

$$V_C = V_{CC} - I_C R_C$$

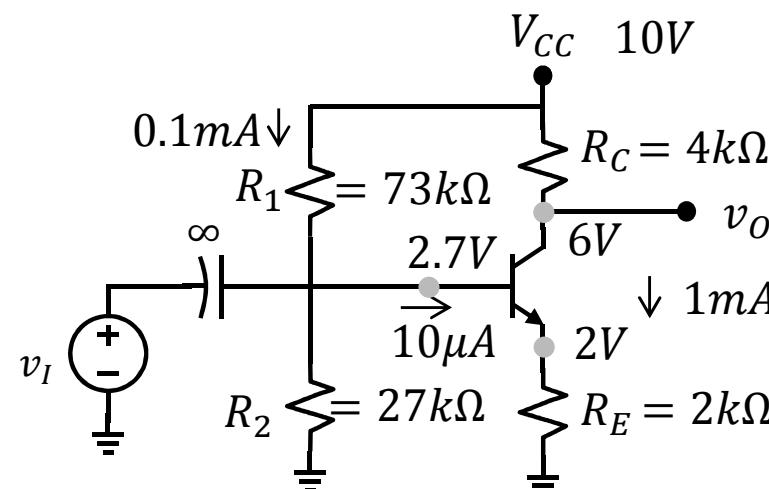


?

This is for design
how about analysis

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

Biasing: $I_E = \text{cte}$


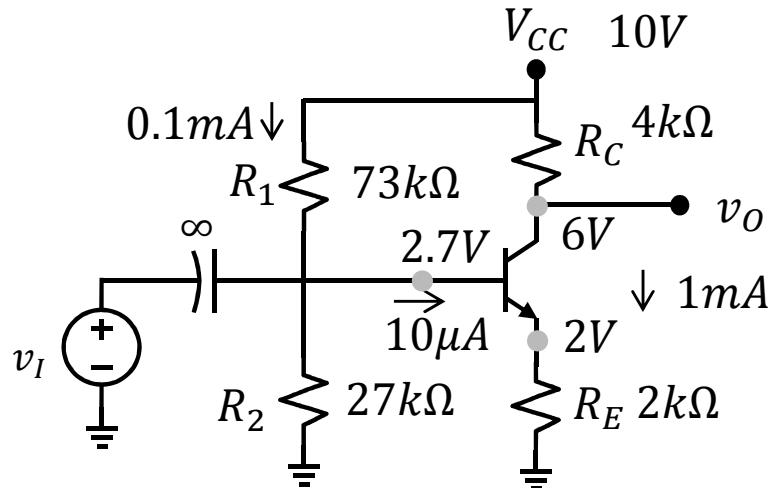


Assume: $I_1 \gg I_B$ $I_1 = 0.1\text{mA}$


$$V_B = 2.7V \quad V_E = 2V$$

$$I_E = 1\text{mA} \quad I_B = 0.01\text{mA}$$

What if β was 10!

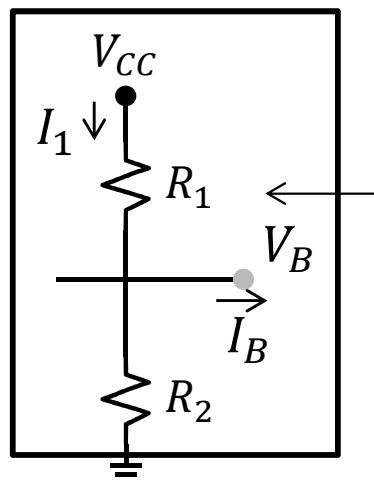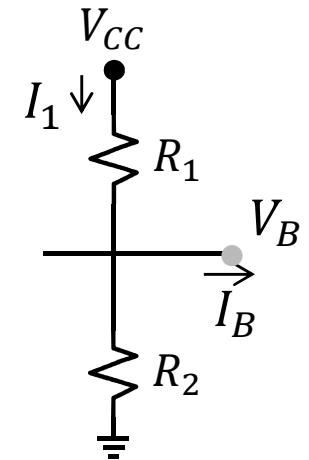

$$V_{CC} \frac{R_2}{R_1 + R_2}$$

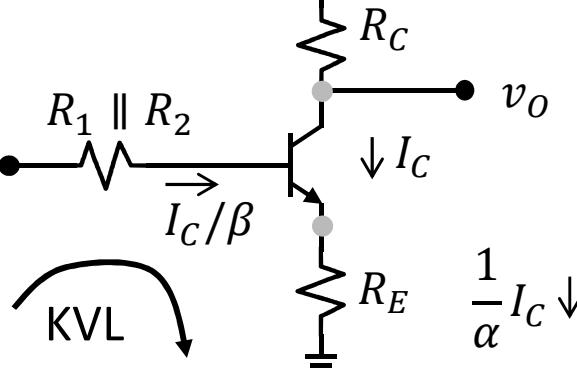


$$\frac{1}{\alpha} I_C \downarrow$$

$$\frac{R_2}{R_1 + R_2} V_{CC} = I_C \frac{R_1 \parallel R_2}{\beta} + V_{BEon} + \frac{1}{\alpha} R_E I_C \quad \rightarrow I_C = \dots$$

For the above numbers: $I_C = \frac{2}{1.01 \times 2k + 0.01 \times 19.7k} = 0.92\text{mA}$


- | | |
|---------------|-------|
| 1. Lab | □□□□ |
| 2. Power | □□□□ |
| 3. Ser/Parl | □□□□□ |
| 4. Small sig. | □□□□□ |
| 5. Applic | □□□□□ |

Biasing: $I_E = \text{cte}$

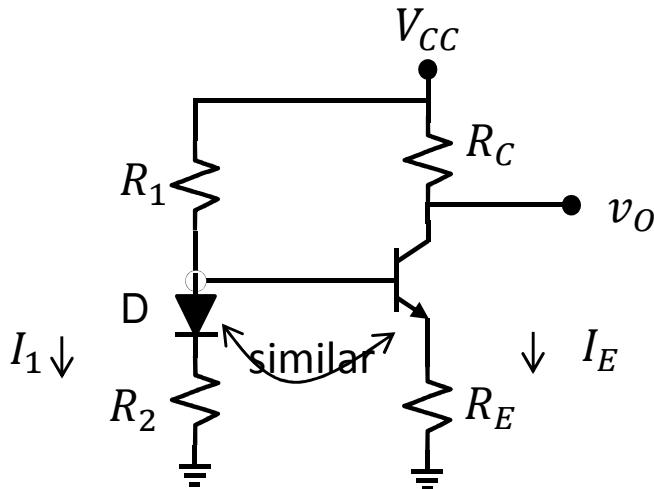


$$I_1 R_2 + V_D = V_{BEon} + I_E R_E$$
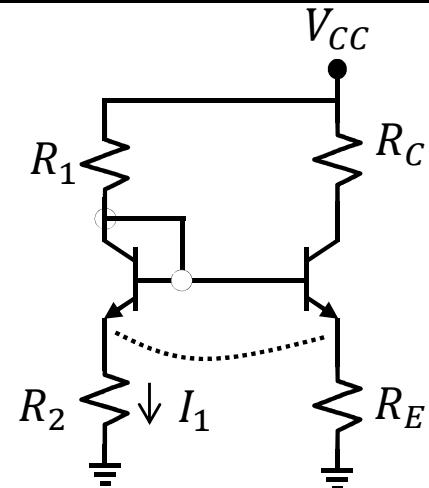
$$I_1 \approx \frac{V_{CC}}{R_1 + R_2} \quad I_E = \frac{R_E}{R_2} I_1$$



$$I_1 R_2 = I_E R_E$$
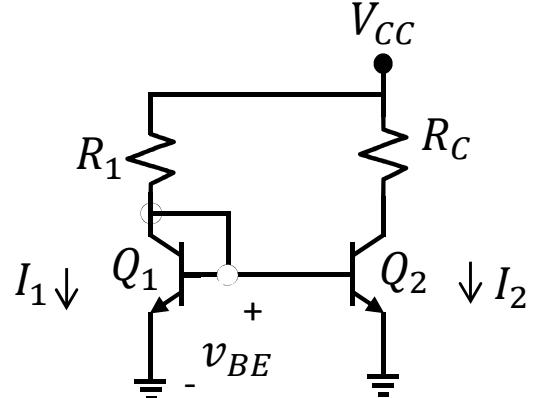
$$I_1 = \frac{V_{CC} - V_{BEon}}{R_1 + R_2}$$



$$I_1 = \frac{V_{CC} - V_{BEon}}{R_1}$$

$$I_1 = I_{S1} (e^{v_{BE}/V_T} - 1)$$


$$I_2 = I_{S2} (e^{v_{BE}/V_T} - 1)$$

$$\frac{I_2}{I_1} = \frac{I_{S2}}{I_{S1}} = \frac{A_{Q2}}{A_{Q1}}$$


area

Biasing: Example 01

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

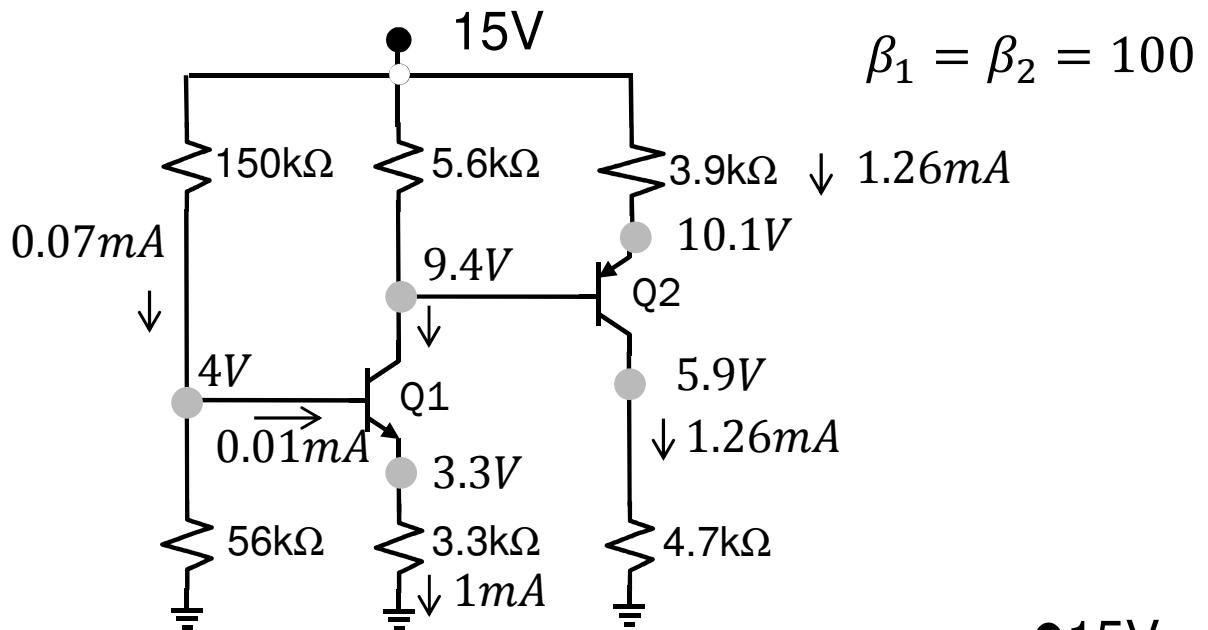

	Q_1	Q_2
I_C [mA]	1	1.26
V_{CE} [V]	6.1	4.2

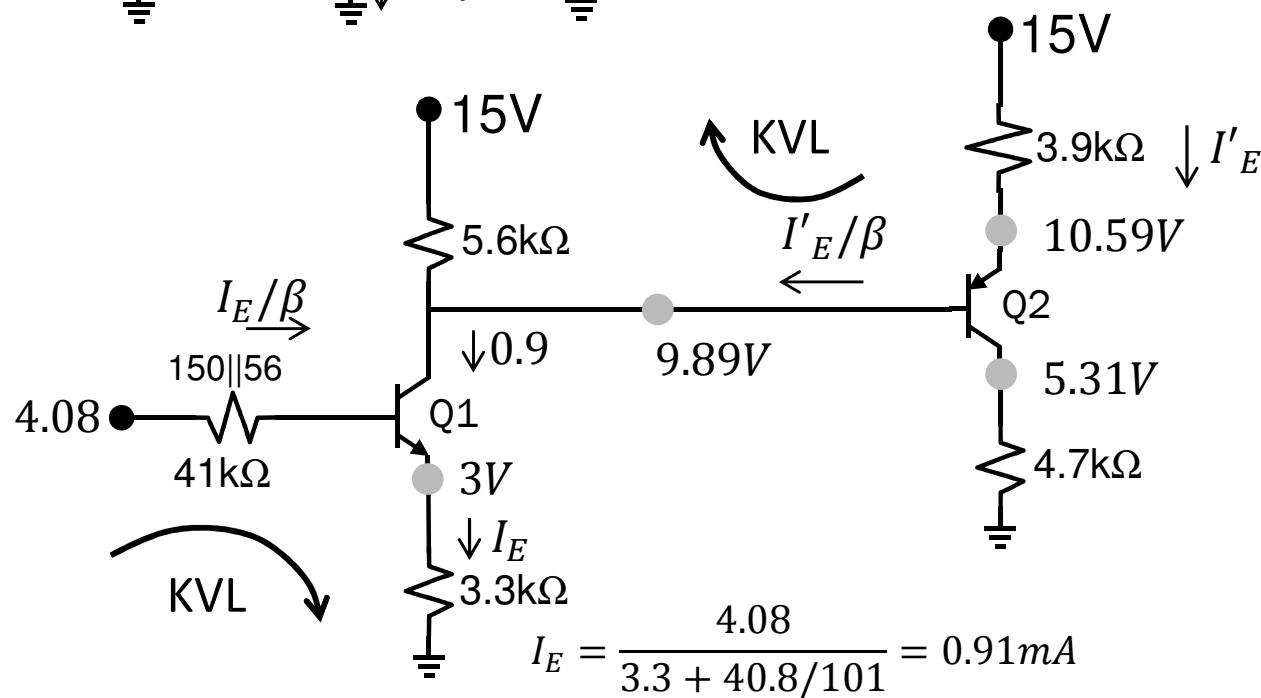


$$3.9I'_E + 0.7 = 5.6(0.9 - \frac{I'_E}{\beta})$$

$$I'_E = 1.13mA$$

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

Biasing: Example 02

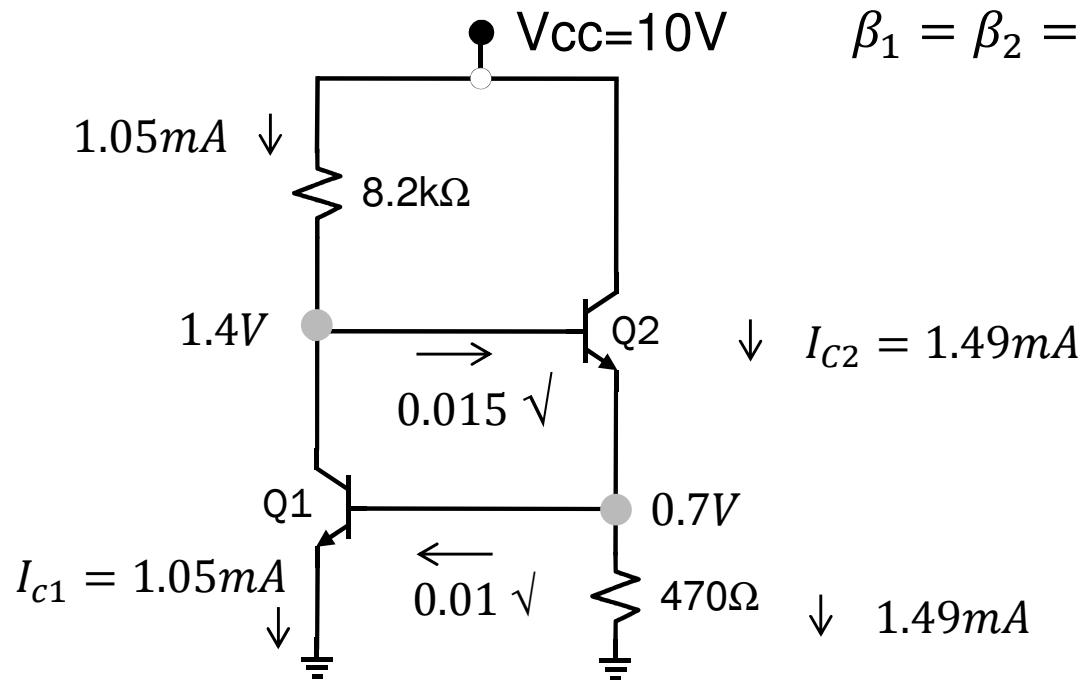


$$\beta_1 = \beta_2 = 100 \quad V_{BEon} = 0.7$$


	Q_1	Q_2
$I_C[\text{mA}]$	1.05	1.49
$V_{CE}[\text{V}]$	1.4	9.3

Biassing: Example 03

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

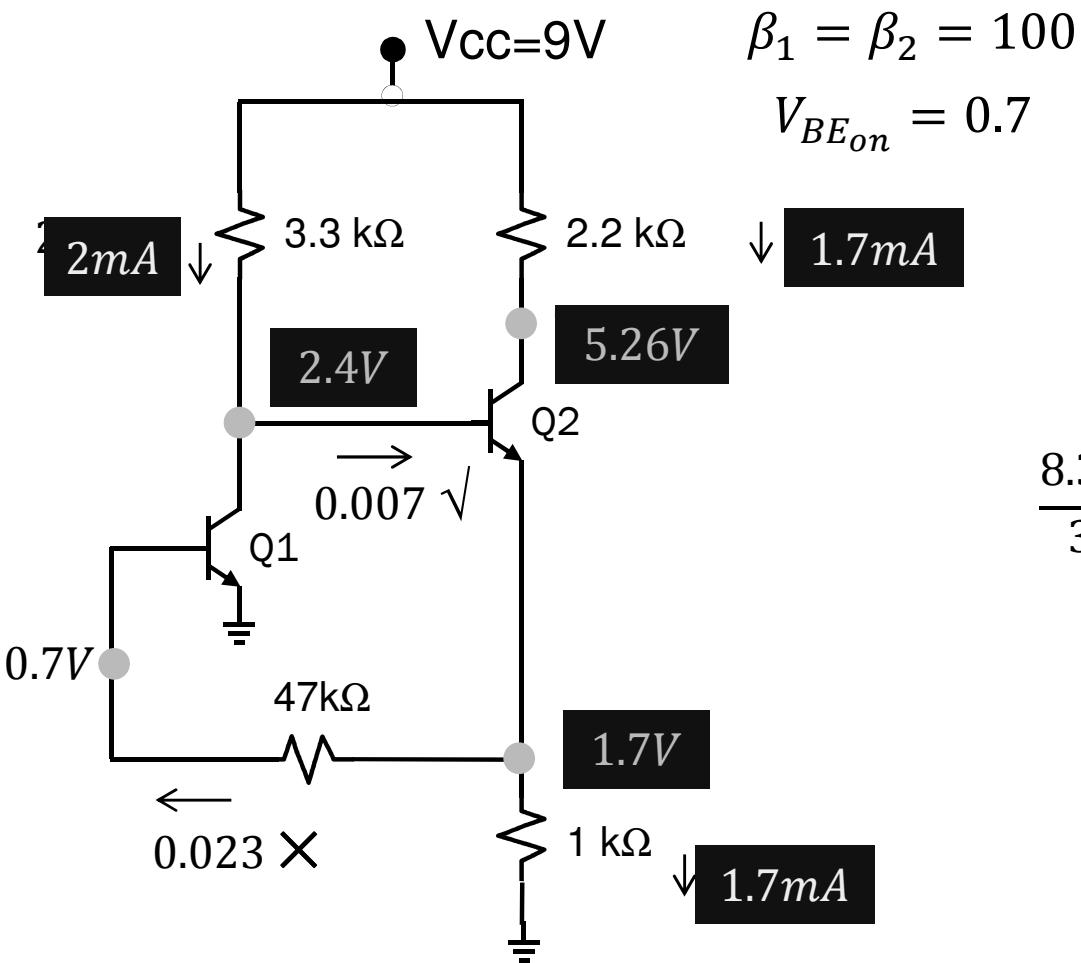



	Q_1	Q_2
$I_C[mA]$	2	1.7
$V_{CE}[V]$	2.4	3.56

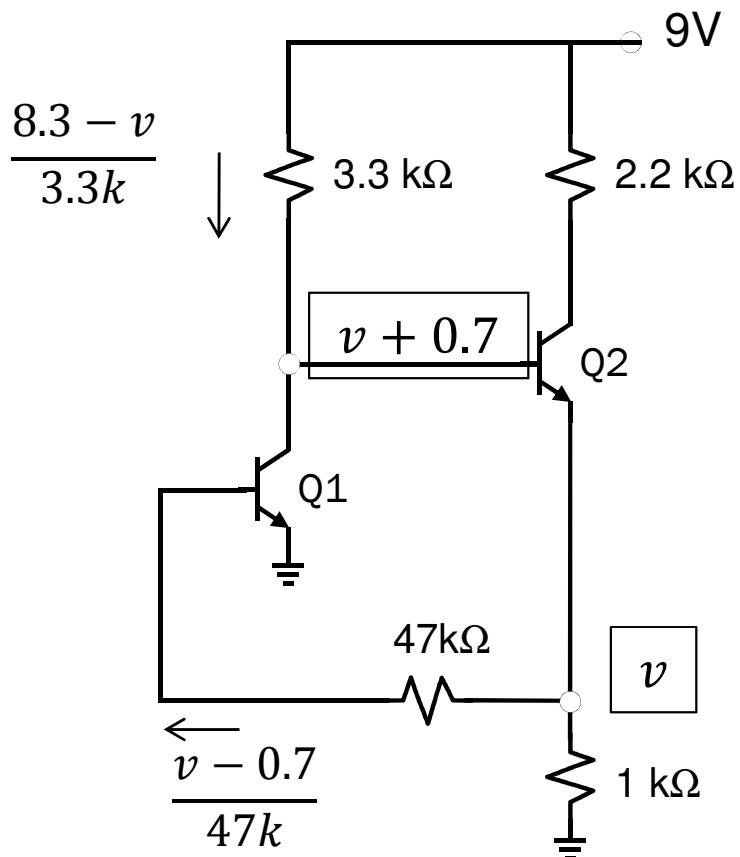

$$\frac{8.3 - v}{330} = \frac{v - 0.7}{47} \Rightarrow v = 1.65$$

Biassing: Example 04

- | | |
|---------------|----------|
| 1. Lab | □□□□ |
| 2. Power | □□□□□ |
| 3. Ser/Parl | □□□□□□ |
| 4. Small sig. | □□□□□□□ |
| 5. Applic | □□□□□□□□ |

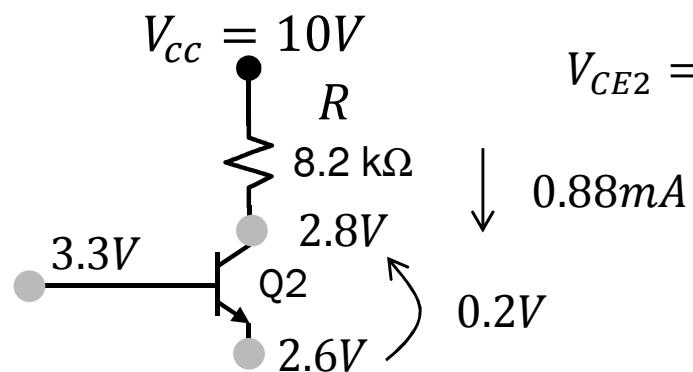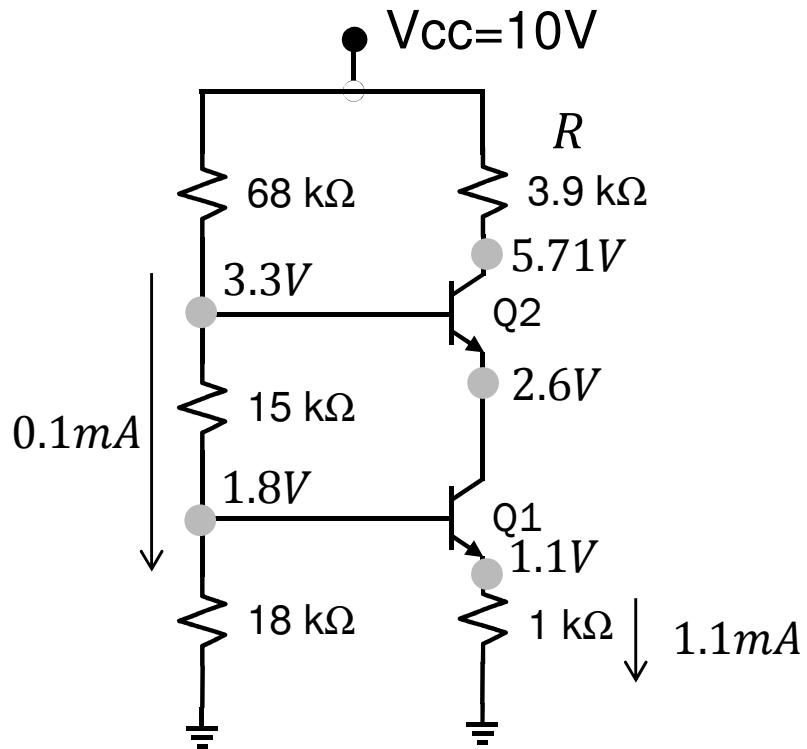


$$V_{CE2} = (10 - 1.1 \times 8.2) - 2.6 \\ = -1.62$$

	Q ₁	Q ₂
I_C [mA]	1.1	0.88
V_{CE} [V]	1.5	0.2

- | | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

Linear BJT Amplifier

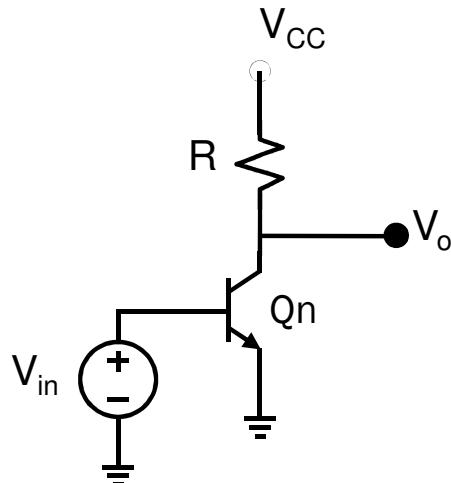

$$V_T = 26mV \quad V_A = 200V$$

$$i_C = I_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right) \approx I_S e^{\frac{v_{BE}}{nV_T}}$$

$$v_{BE} = V_B + \hat{v}_i \sin \omega t$$


$$\begin{aligned} v_O &= V_{CC} - R i_C = V_{CC} - R I_S e^{\frac{V_B}{V_T}} e^{\frac{\hat{v}_i \sin \omega t}{V_T}} \\ &= V_{CC} - R I_C \left(1 + \frac{\hat{v}_i}{V_T} \sin \omega t + \frac{\hat{v}_i^2}{2V_T^2} \sin^2 \omega t + \dots \right) \\ &\approx \underbrace{V_{CC} - R I_C}_{V_O} - \underbrace{R I_C \frac{\hat{v}_i}{V_T} \sin \omega t}_{v_o} \end{aligned}$$

$$A_V = \frac{v_o}{v_{in}} = \frac{-R_C I_C}{V_T} = -g_m R_C$$

$$g_m = \frac{I_C}{V_T}$$


- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

BJT Small Signal Model (h- π)

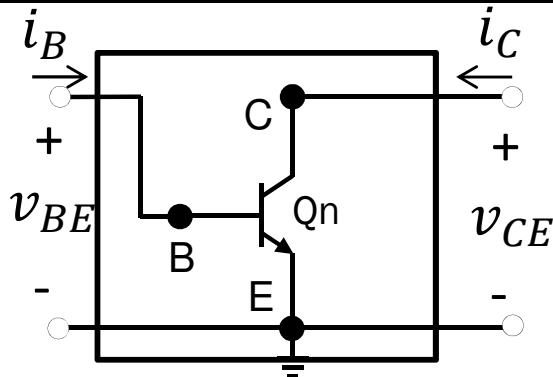

$$i_C = I_S \left(e^{\frac{v_{EB}}{V_T}} - 1 \right) \left(1 + \frac{v_{CE}}{V_A} \right)$$
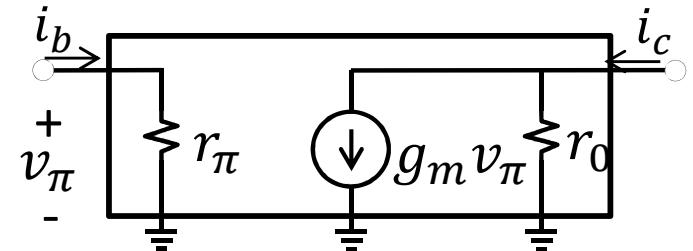
$$\cong \underbrace{I_S e^{\frac{v_{EB}}{V_T}}}_{I_C} \left(1 + \frac{v_{CE}}{V_A} \right)$$



Input resistance:

$$r_\pi \equiv \frac{\partial v_{BE}}{\partial i_B} = \left(\frac{\partial i_C}{\partial v_{BE}} \right)^{-1} = \beta \left(\frac{\partial i_C}{\partial v_{BE}} \right)^{-1} = \beta \left(\frac{I_S}{V_T} e^{\frac{v_{EB}}{V_T}} \right)^{-1} = \beta \frac{V_T}{I_C} = \frac{\beta}{g_m} = \beta r_m$$

Output resistance:


$$r_o \equiv \frac{\partial v_{CE}}{\partial i_C} = \left(\frac{\partial i_C}{\partial v_{CE}} \right)^{-1} = \left(\frac{I_C}{V_A} \right)^{-1} = \frac{V_A}{I_C}$$

Trans-Conductance:

$$g_m \equiv \frac{\partial i_C}{\partial v_{BE}} = \frac{I_S}{V_T} e^{\frac{v_{EB}}{V_T}} = \frac{I_C}{V_T} = \frac{1}{r_m}$$

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

Example 01 - CE

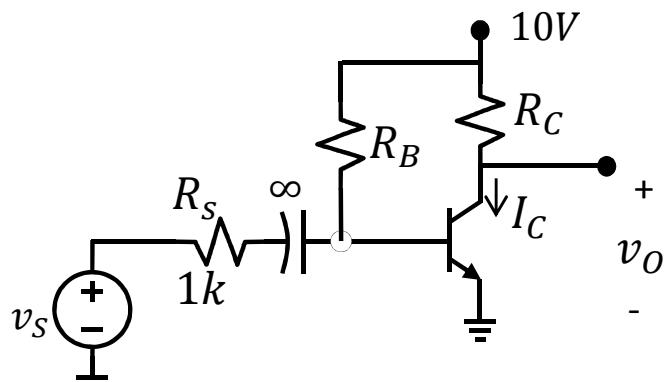


DC: $R_B = \frac{10 - 0.7}{0.01mA} = 930k\Omega$

Assume $\beta = 100$ $V_A \sim \infty$


Design for $I_C = 1mA$ and maximum swing

Find A_v, R_{in}, R_{out}

window
for v_o

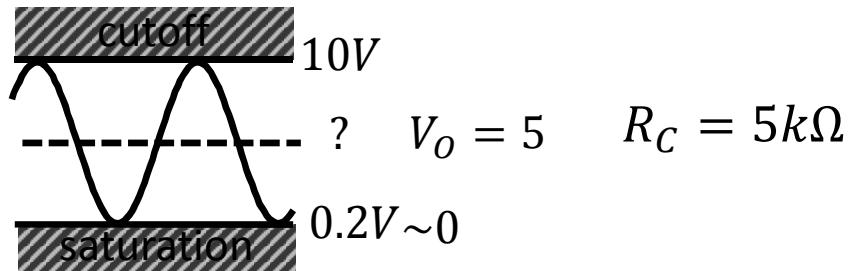

AC:

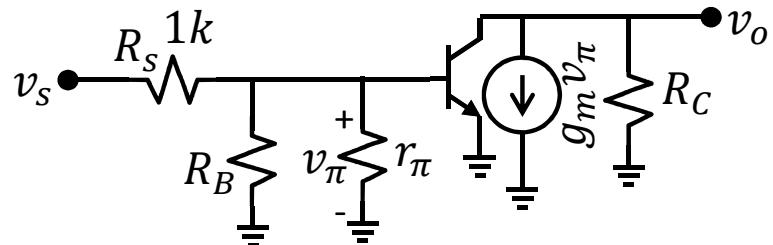

$$v_\pi = v_s \frac{r_\pi \parallel R_B}{r_\pi \parallel R_B + R_s} \sim v_s \frac{r_\pi}{r_\pi + R_s}$$


$$v_o = -g_m v_\pi R_C$$

$$A_v = \frac{v_0}{v_s} = -g_m R_C \frac{r_\pi}{r_\pi + R_s} = \frac{-\beta R_C}{r_\pi + R_s} = \frac{-R_C}{r_m + R_s/\beta} = -\frac{\text{Collector resistance}}{\text{Emitter's circuit resistance}}$$

if $R_s \rightarrow 0$: $A_v = -g_m R_C$


Example 02 - CE

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

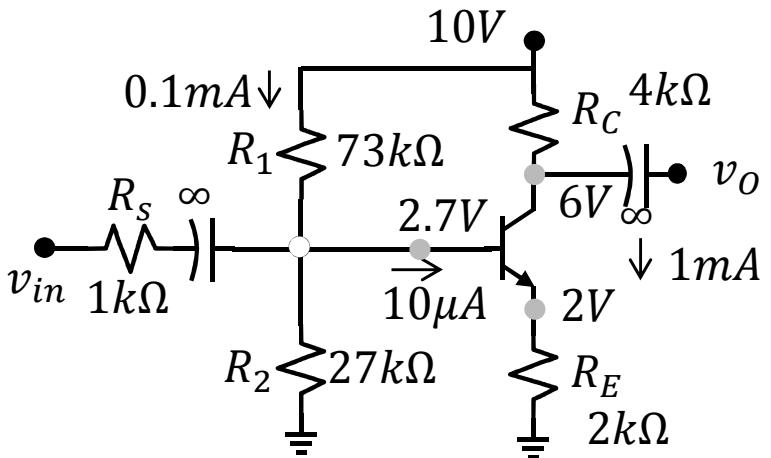

Assume $\beta = 100$ $V_A \sim \infty$ Find A_v, R_{in}, R_{out}


AC circuit

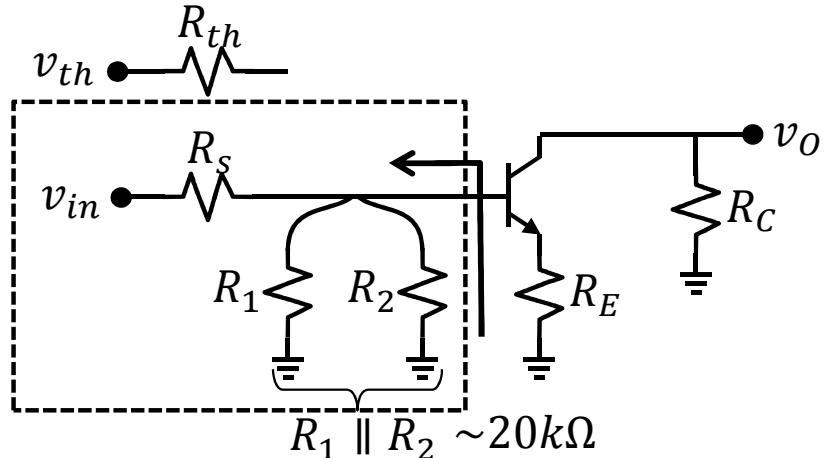

$$v_{th} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s} v_{in} \quad R_{th} = R_1 \parallel R_2 \parallel R_s$$

$$KVL: -v_{th} + R_{th} \frac{v_\pi}{r_\pi} + v_\pi + R_E \frac{v_\pi}{r_\pi} (1 + \beta) = 0$$
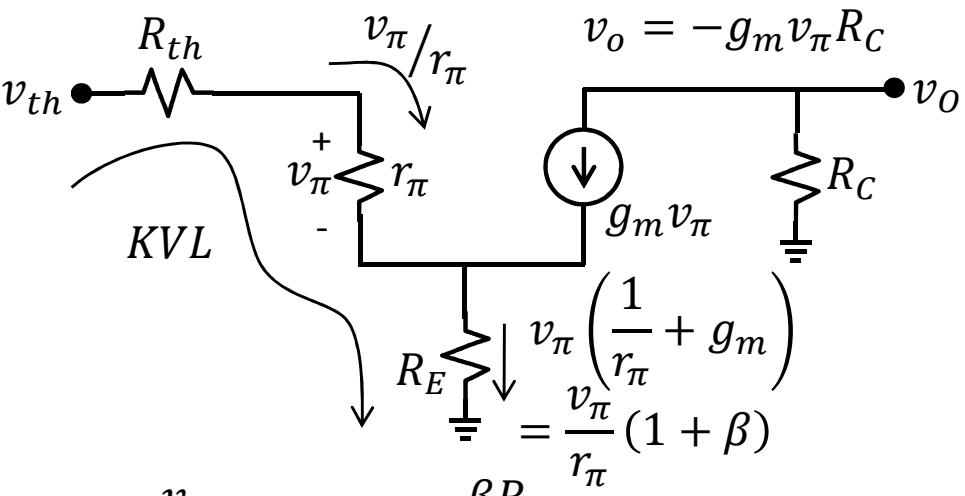
$$v_\pi = v_{th} \frac{r_\pi}{R_{th} + r_\pi + R_E(1 + \beta)}$$




$$\begin{aligned} A'_v &= \frac{v_o}{v_{th}} = \frac{-\beta R_C}{R_{th} + r_\pi + R_E(1 + \beta)} \\ &= \frac{R_{th} + r_\pi}{\beta} + R_E \left(\frac{1 + \beta}{\beta} \right) \end{aligned}$$


$$A_v = \frac{v_o}{v_s} = \frac{v_{th}}{v_s} \cdot \frac{v_o}{v_{th}} = -\frac{20}{21} \cdot \frac{4}{\frac{3.5}{100} + 2 \times \frac{101}{100}} = -1.8$$

Example 02 - CE


- | | |
|---------------|----------|
| 1. Lab | □□□□ |
| 2. Power | □□□□ |
| 3. Ser/Parl | □□□□□□ |
| 4. Small sig. | □□□□□□ |
| 5. Applic | □□□□□□□□ |

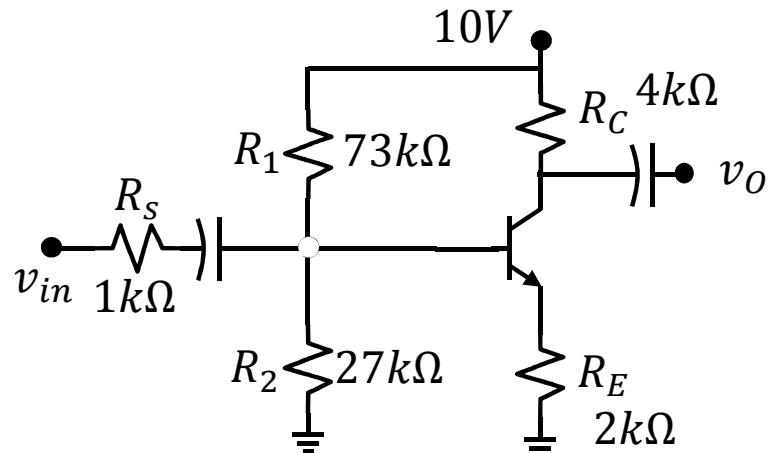

$$A_v = -1.8$$

 


How we can increase gain?

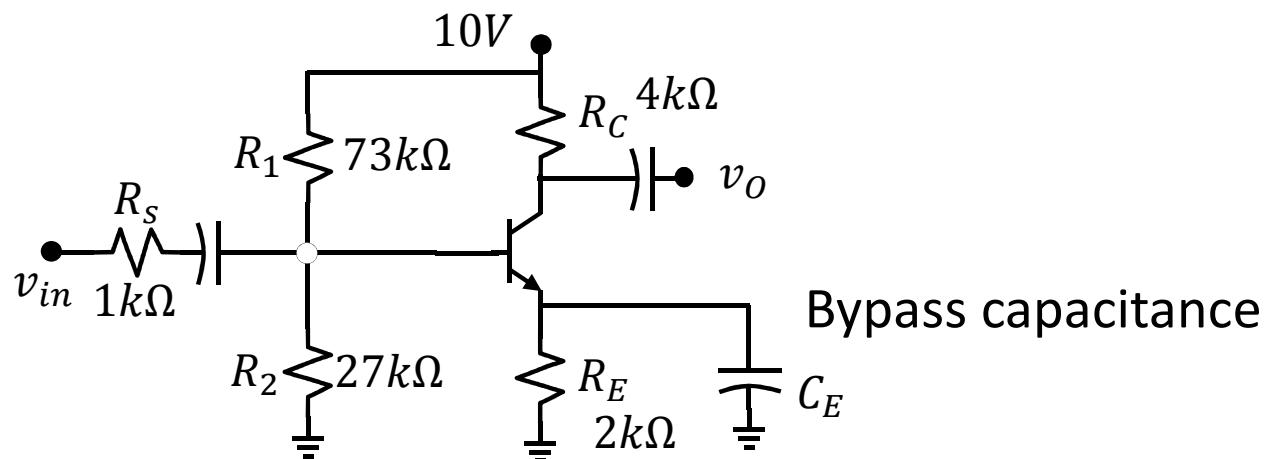



Example 03 - CC

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

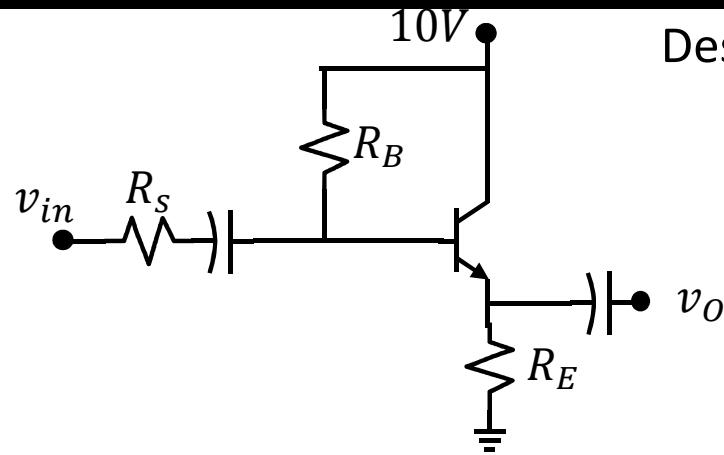

Design a buffer $I_C = 1mA$

AC circuit

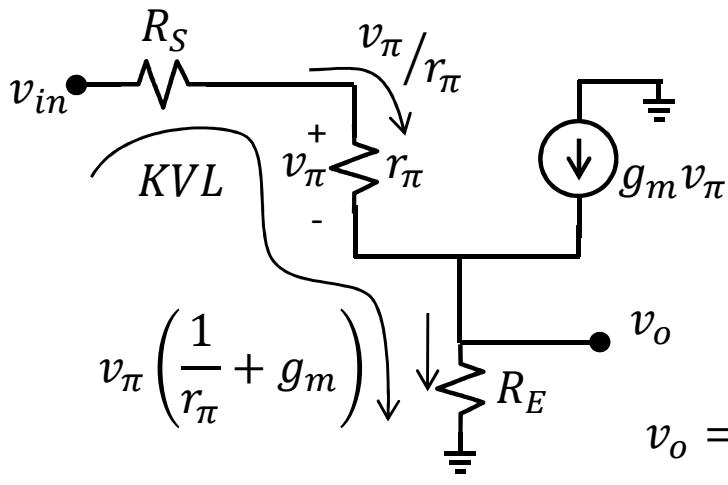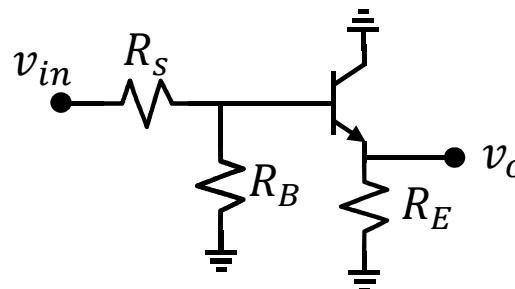

KVL:


$$-v_{in} + R_S \frac{v_\pi}{r_\pi} + v_\pi + R_E \left(\frac{v_\pi}{r_\pi} + g_m v_\pi \right) = 0$$

$$v_o = v_\pi \left(\frac{1}{r_\pi} + g_m \right) R_E$$

$$v_\pi = \frac{v_{in}}{\frac{R_S}{r_\pi} + 1 + R_E \left(g_m + \frac{1}{r_\pi} \right)}$$

$$A_v = \frac{v_o}{v_{in}} = \frac{\left(\frac{1}{r_\pi} + g_m \right) R_E}{\frac{R_S}{r_\pi} + 1 + R_E \left(g_m + \frac{1}{r_\pi} \right)} = \frac{R_E}{\frac{R_S + r_\pi}{1 + \beta} + R_E} \sim 1$$

window for v_E

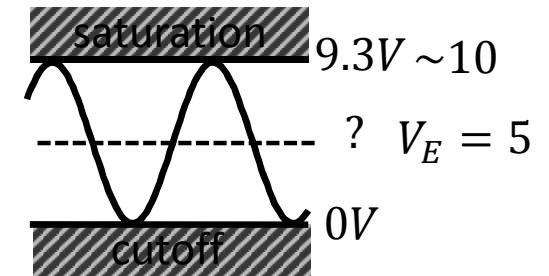


$$R_E = 5k\Omega$$


$$R_B = \frac{10 - 5.7}{0.01m} = 430k\Omega$$

Example 03 - CC


- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

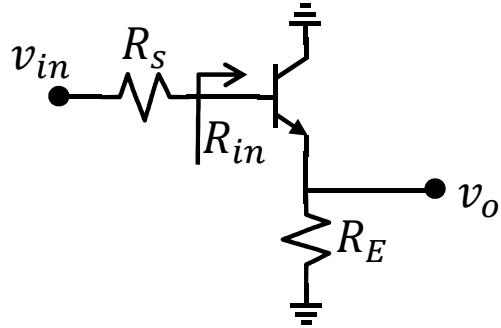
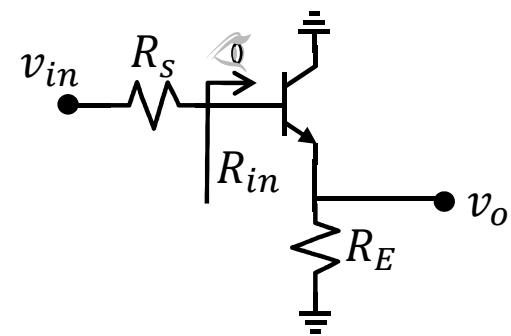
$$\frac{v_o}{v_{in}} = \frac{R_E}{\frac{R_S + r_\pi}{1 + \beta} + R_E}$$




$$R_{in} = r_\pi + R_E(1 + \beta)$$

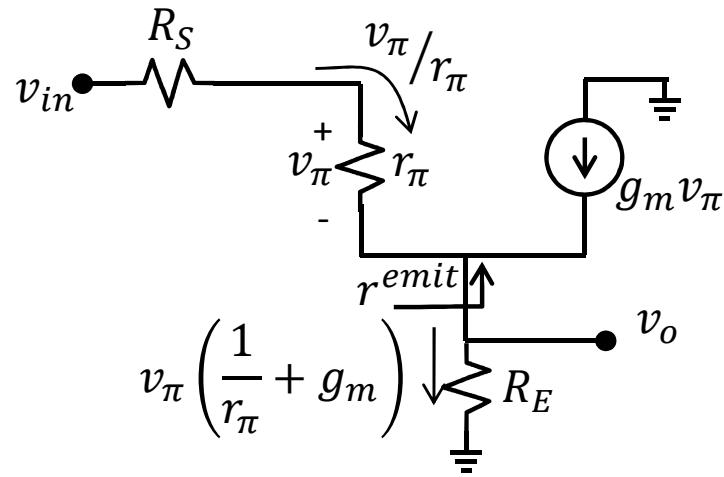

$$R_{in} = \frac{v_\pi + R_E \left(\frac{v_\pi}{r_\pi} + g_m v_\pi \right)}{\frac{v_\pi}{r_\pi}}$$

$$= r_\pi + R_E(1 + \beta)$$

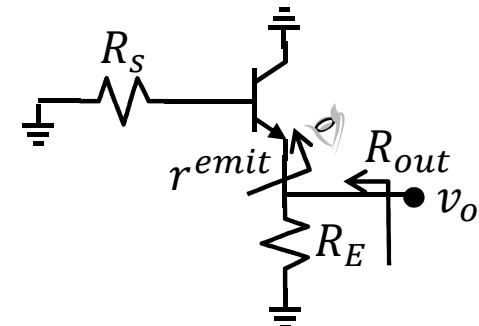


$$R_{out} = R_E \parallel r_{emit}$$

$$= R_E \parallel \frac{R_S + r_\pi}{1 + \beta}$$

Example 04 – Multi-stage Amplifier

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

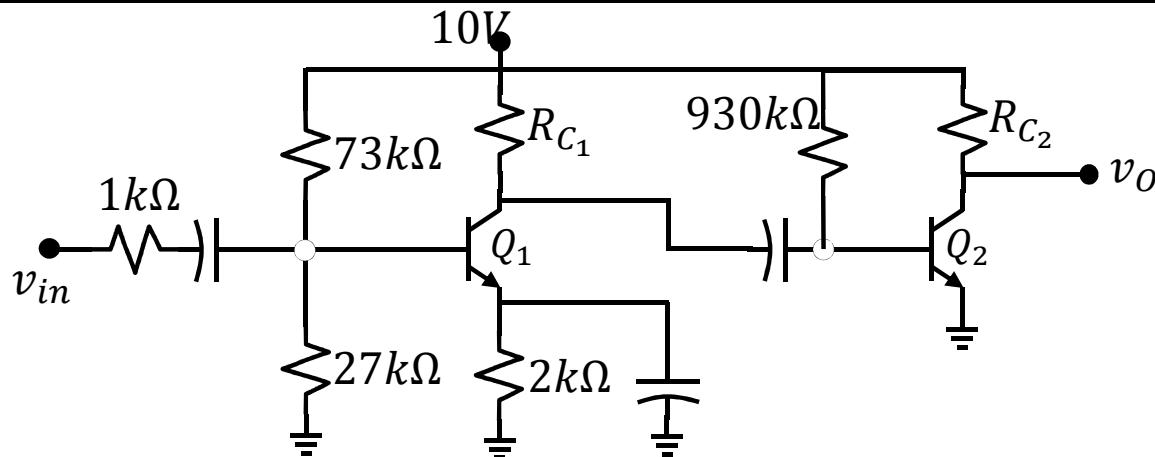


Design an amplifier:

$$\begin{aligned} I_C &= 1mA \\ \beta &= 100 \\ A_v &\geq 1000 \\ V_{cc} &= 10V \\ R_S &= 1k\Omega \end{aligned}$$

$$R_{C_1} = \frac{10 - 3}{1m} = 7k\Omega$$

$$R_{C_2} = \frac{10 - 5}{1m} = 5k\Omega$$

AC circuit

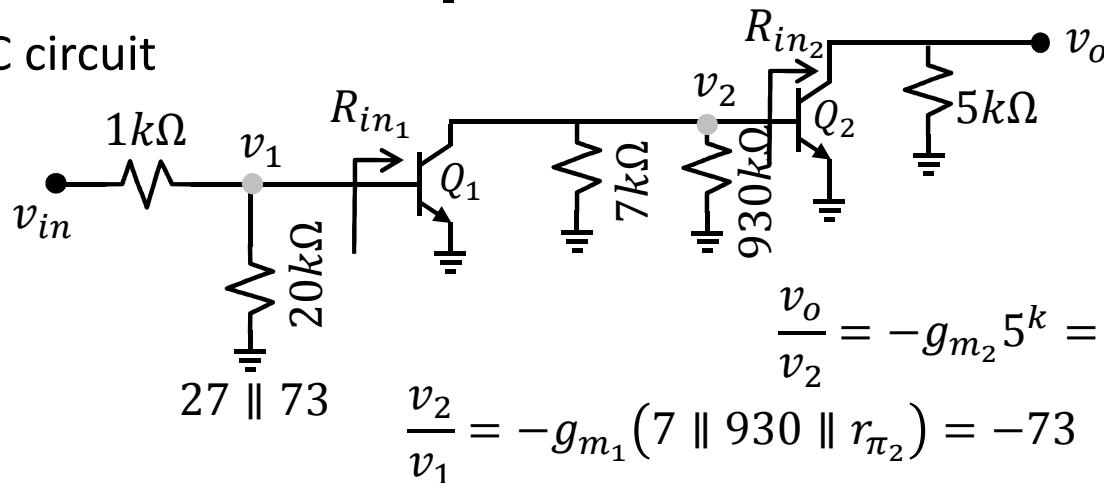


$$A_v = \frac{v_o}{v_i} = \frac{v_1}{v_i} \cdot \frac{v_2}{v_1} \cdot \frac{v_o}{v_2}$$

$$A_v = 10143$$

$$\frac{v_1}{v_i} = \frac{20^k \parallel r_{\pi_1}}{20^k \parallel r_{\pi_1} + 1^k} = 0.69$$


$$\frac{v_2}{v_1} = -g_{m_1}(7 \parallel 930 \parallel r_{\pi_2}) = -73$$

$$\frac{v_o}{v_2} = -g_{m_2} 5^k = -200$$

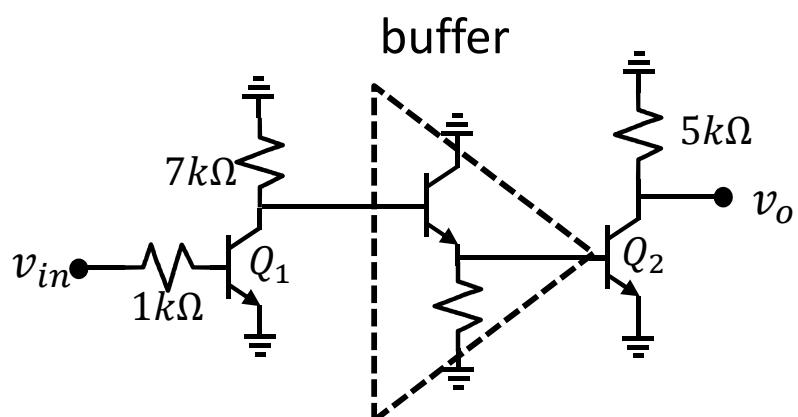


Example 05 – CE , CB, CC


- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

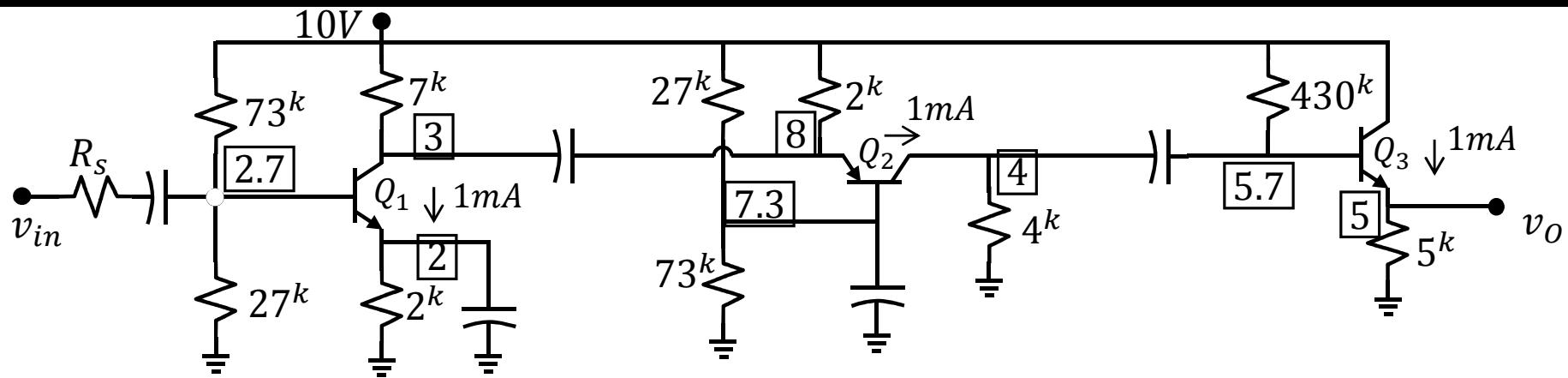

AC circuit

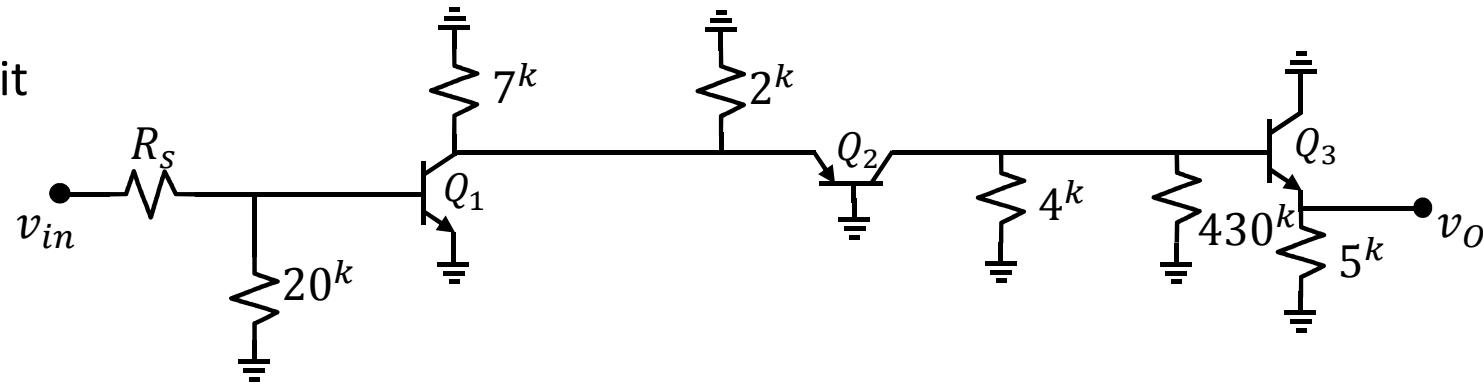


$R_s \ll ?$

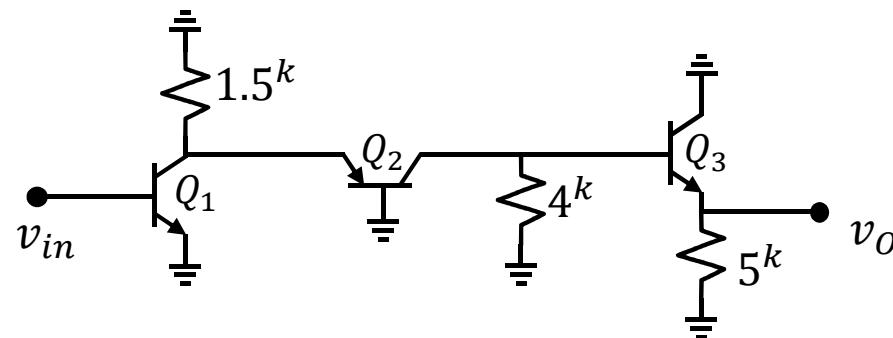

Common Base

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

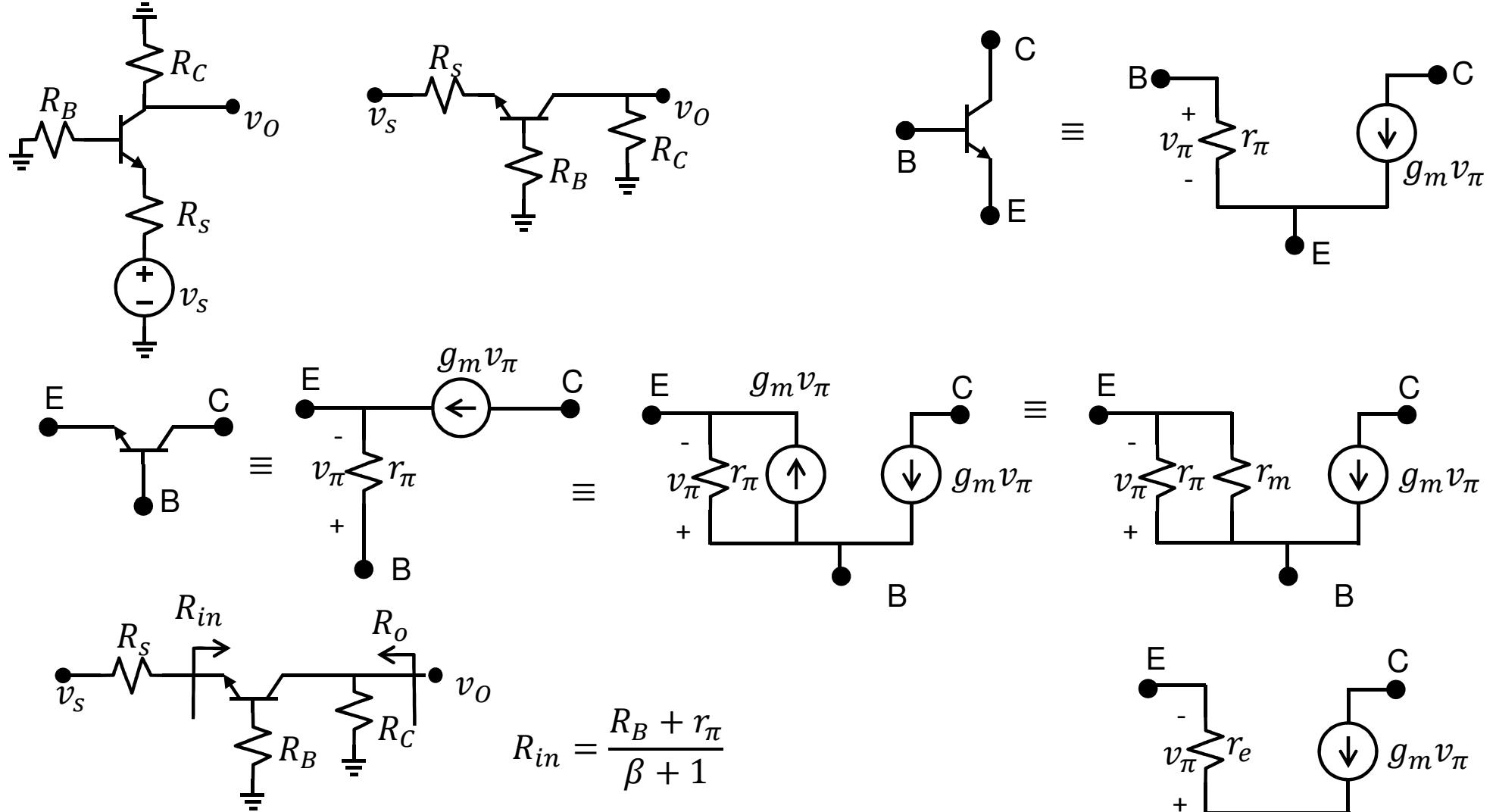


$$A_v = \frac{v_o}{v_s} = \frac{R_c}{\frac{R_B + r_\pi}{\beta + 1} + R_s}$$

$$R_o = R_c$$

$$r_e = r_m \parallel r_\pi = r_m \frac{\beta}{\beta + 1} \cong r_m$$

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

Example 05 – CE , CB, CC

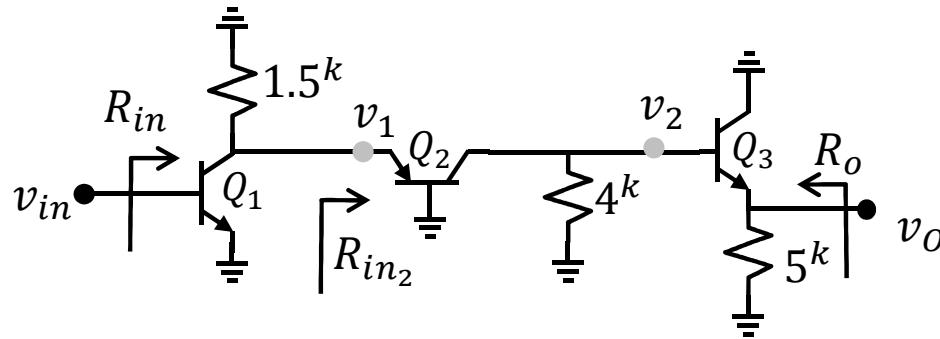

$$\frac{v_1}{v_s} \approx r_m = -g_m (1.5^k \parallel R_{in2}) = -1$$

$$\frac{v_2}{v_1} = +g_m (4^k \parallel (r_{\pi_2} + \beta 5^k)) = 160$$

$$\frac{v_o}{v_2} = \frac{5^k}{5^k + \frac{r_{\pi_2}}{\beta}} \cong 1$$


$$A_v = \frac{v_o}{v_s} = \frac{v_1}{v_s} \cdot \frac{v_2}{v_1} \cdot \frac{v_o}{v_2} = -160$$

$$R_{in} = r_{\pi_1} = 2.5^k$$


$$R_o = 4^k \parallel \frac{4^k + r_{\pi_2}}{\beta + 1} = 63\Omega$$

Cascode Amplifier , CE-CB

- | | | | |
|---------------|-------------------------------------|-------------------------------------|-------------------------------------|
| 1. Lab | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. Power | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 3. Ser/Parl | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 4. Small sig. | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |
| 5. Applic | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> | <input checked="" type="checkbox"/> |

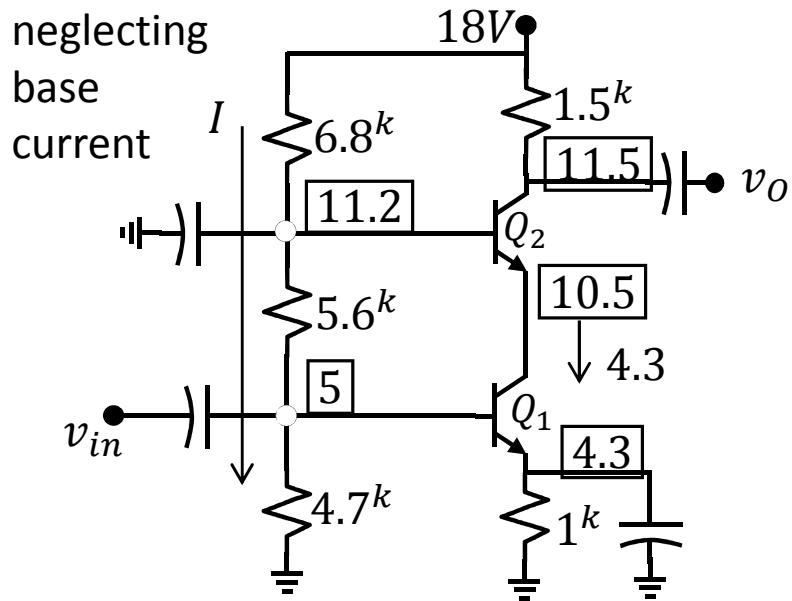

AC circuit:

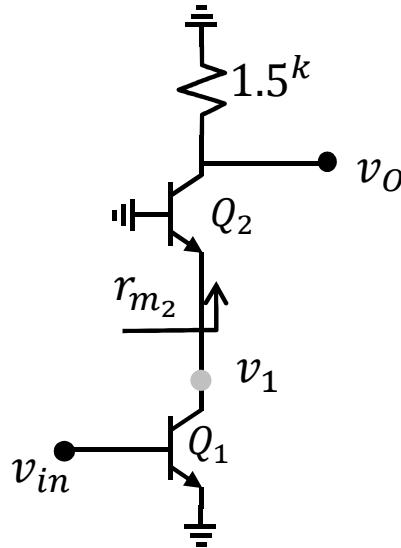

$$I = \frac{18}{6.8 + 5.6 + 4.7} = 1.1 \text{ mA}$$





$$\frac{v_1}{v_{in}} = -g_m(r_{m2}) = -1$$

$$\frac{v_o}{v_1} = \frac{1.5k}{r_{\pi_2}/\beta} = 245$$

$$A_v = -245$$


Some Notes:

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

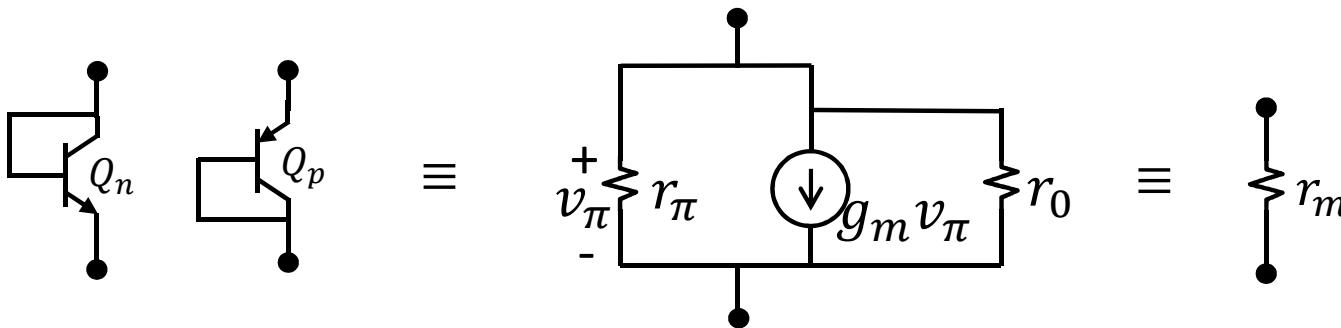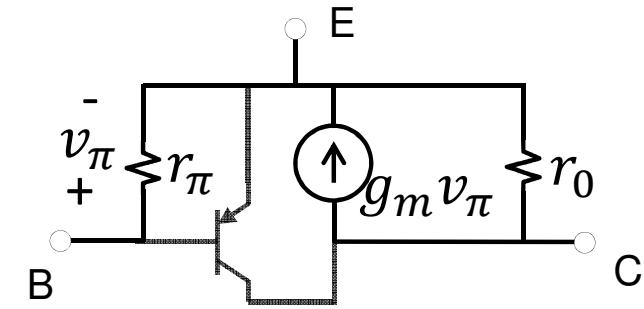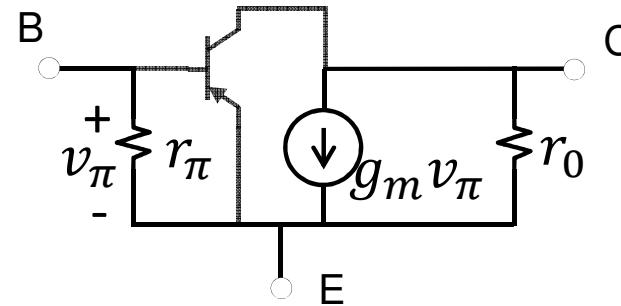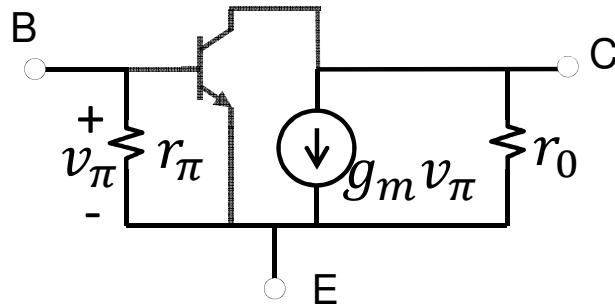

Summary


- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

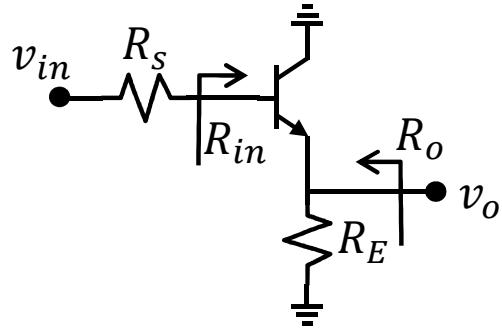

$$\frac{v_o}{v_{in}} = \frac{R_E}{\frac{R_s + r_\pi}{1 + \beta} + R_E}$$

$$R_{in} = r_\pi + R_E(1 + \beta)$$

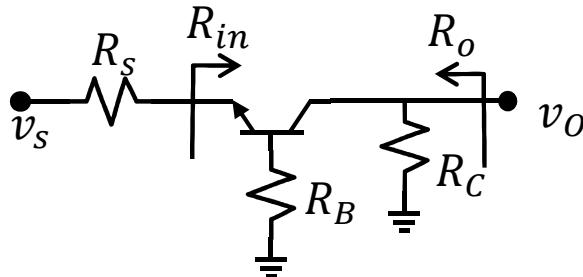
$$R_o = R_E \parallel \frac{R_s + r_\pi}{1 + \beta}$$



$$\frac{v_o}{v_s} = \frac{R_C}{\frac{R_B + r_\pi}{\beta + 1} + R_s}$$

$$R_{in} = \frac{R_B + r_\pi}{\beta + 1}$$

$$R_o = R_c$$

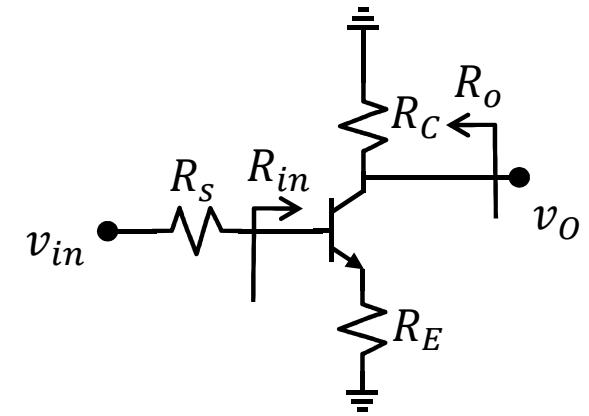


$$\frac{v_o}{v_s} = \frac{-R_C}{\frac{R_s + r_\pi}{\beta + 1} + R_E}$$

$$R_{in} = r_\pi + R_E(1 + \beta)$$

$$R_o = R_C$$

? V_A


- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |
-

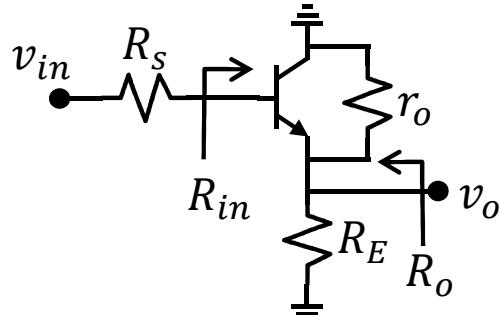

$$r_o = \infty$$

$$\frac{v_o}{v_{in}} = \frac{R_E}{\frac{R_S + r_\pi}{1 + \beta} + R_E}$$

$$R_{in} = r_\pi + R_E(1 + \beta)$$

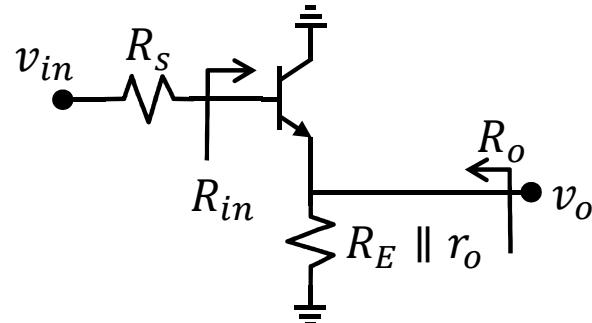

$$\frac{v_o}{v_{in}} = \frac{R_E \parallel r_o}{\frac{R_S + r_\pi}{1 + \beta} + R_E \parallel r_o}$$




$$R_{in} = r_\pi + (R_E \parallel r_o)(1 + \beta)$$

$$R_o = R_E \parallel \frac{R_S + r_\pi}{1 + \beta}$$



$$R_o = R_E \parallel r_o \parallel \frac{R_S + r_\pi}{1 + \beta}$$

Input / Output Impedances

- | | |
|---------------|--|
| 1. Lab | |
| 2. Power | |
| 3. Ser/Parl | |
| 4. Small sig. | |
| 5. Applic | |

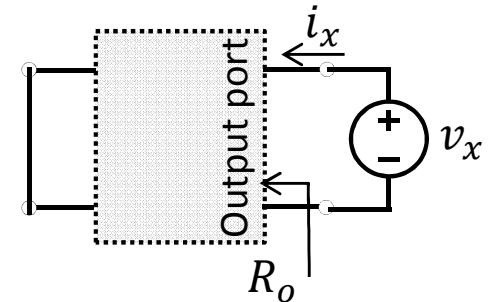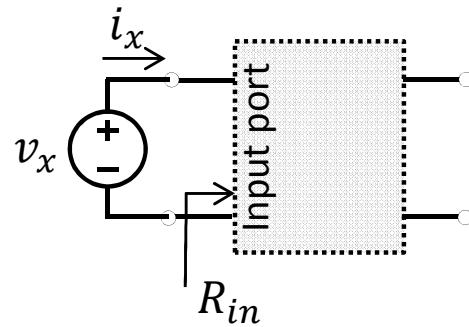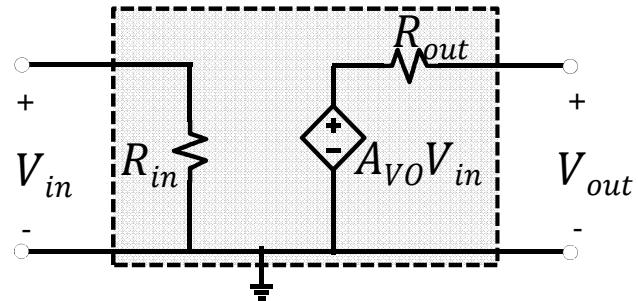

DC Analysis

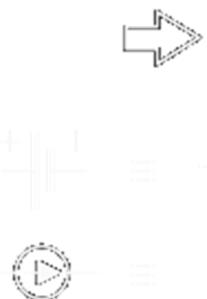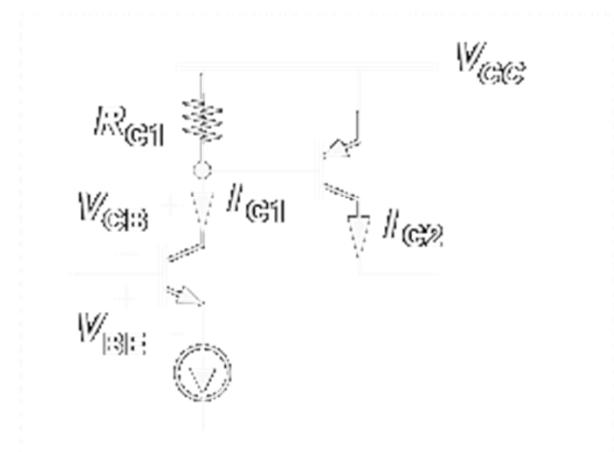

Small-Signal Analysis

