

سوال 1 تمرین های کلاس تمرین

(الف)

$$\int_{-\infty}^{\infty} \delta(\alpha x) dx = \int_{-\infty}^{\infty} \delta(u) \frac{du}{|\alpha|} = \frac{1}{|\alpha|}$$

and so

$$\delta(\alpha x) = \frac{\delta(x)}{|\alpha|}.$$

Let $x = \sqrt{u}$, so $dx = \frac{du}{2\sqrt{u}}$, then

(ب)

$$\int_0^{\infty} f(x) \delta(x^2 - a^2) dx = \int_0^{\infty} \frac{f(\sqrt{u})}{2\sqrt{u}} \delta(u - a^2) du = \frac{f(|a|)}{2|a|}.$$

Let $x = -\sqrt{u}$, so $dx = -\frac{du}{2\sqrt{u}}$, then

$$\int_{-\infty}^0 f(x) \delta(x^2 - a^2) dx = \int_0^{\infty} \frac{f(-\sqrt{u})}{2\sqrt{u}} \delta(u - a^2) du = \frac{f(-|a|)}{2|a|}.$$

Hence

$$\int_{-\infty}^{\infty} f(x) \delta(x^2 - a^2) dx = \frac{1}{2|a|} (f(|a|) + f(-|a|)) = \frac{1}{2|a|} (f(a) + f(-a)).$$

سوال 1 تمرین های کلاس تمرین

(ج)

$$I = \int_{-\infty}^{\infty} t\delta'(t) dt = t\delta(t)|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} \delta(t) dt = - \int_{-\infty}^{\infty} \delta(t) dt = \int_{-\infty}^{\infty} (-\delta(t)) dt$$

$$\rightarrow t\delta'(t) = -\delta(t)$$

$$\text{Hint: } f(x) = x, x_0 = 0, \int_{-\infty}^{\infty} f(x)\delta(x - x_0) dx = f(x_0) \rightarrow \int_{-\infty}^{\infty} x\delta(x) dx = 0 \Rightarrow t\delta(t) = 0$$


(د)

$$I = \int_{-\infty}^{\infty} f(x)\delta'(x) dx = f(x)\delta(x)|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} f'(x)\delta(x) dx = -f'(0)$$

$$\text{Hint: } f(x) = 0 \text{ for } |x| < b \text{ and } x_0 = 0, \int_{-\infty}^{\infty} f(x)\delta(x) dx = f(0) \rightarrow \int_{-\infty}^{\infty} f(x)\delta(x) dx = 0$$

$$\text{So } f(x)\delta(x) = 0.$$


١-الف

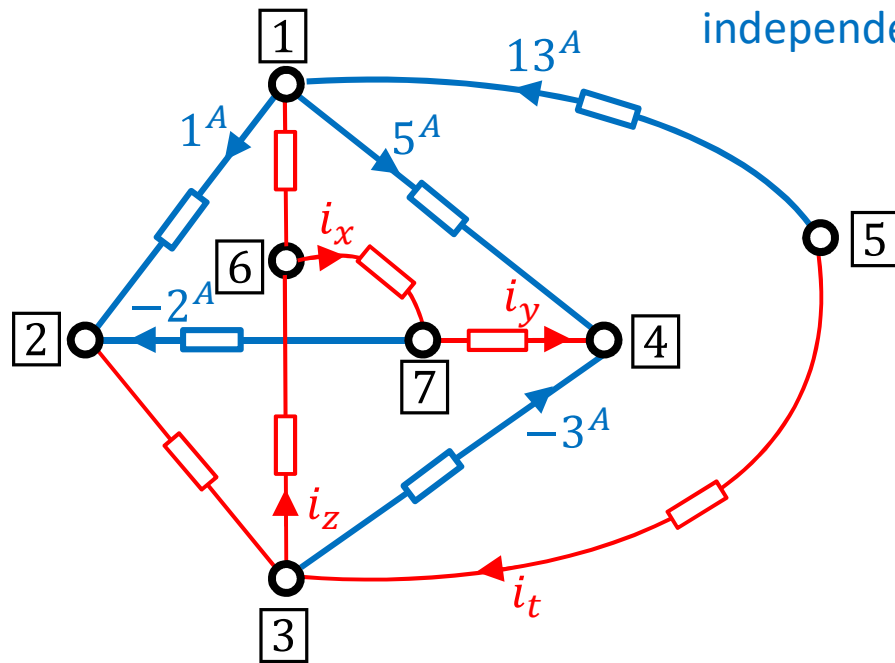

independent current variables

- [5]: $i_t = -13^A$
- [4]: $i_y = 3 - 5 = -2^A$
- [7]: $i_x = -2 - 2 = -4^A$
- [2]: $i_{2 \rightarrow 3} = 1 - 2 = -1^A$
- [3]: $i_z = -13 + 3 - 1 = -11^A$

ب-١


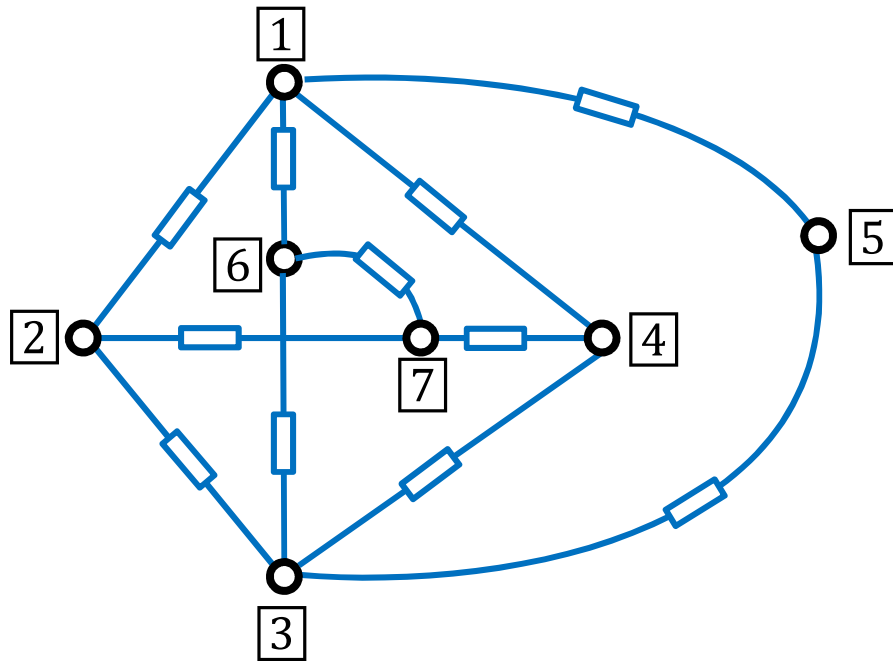


of branches = 11 \rightarrow # unknown currents = 11



of nodes = 7 \rightarrow # independent KCL equations = 6

\rightarrow # of independent current variables = $11 - 6 = 5$


١٠

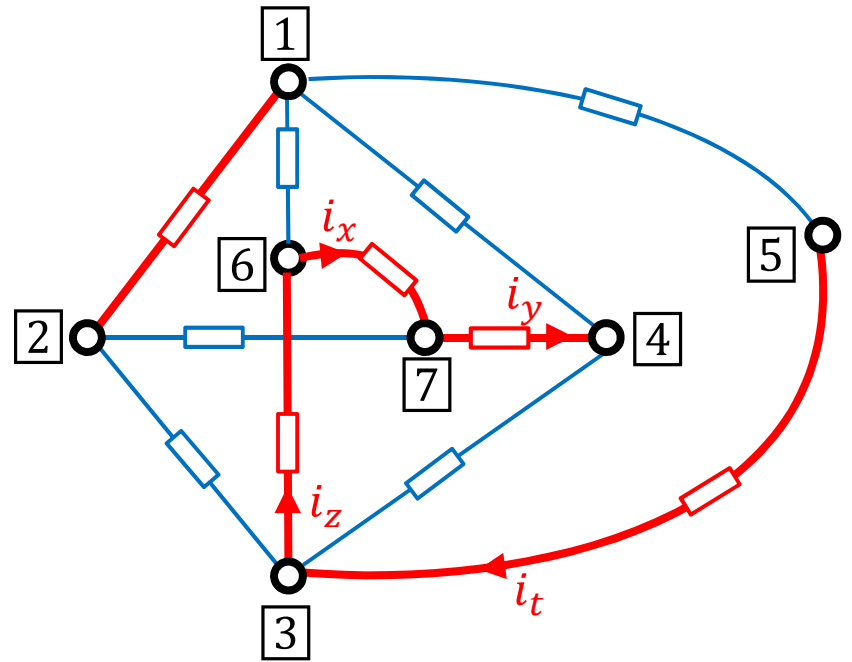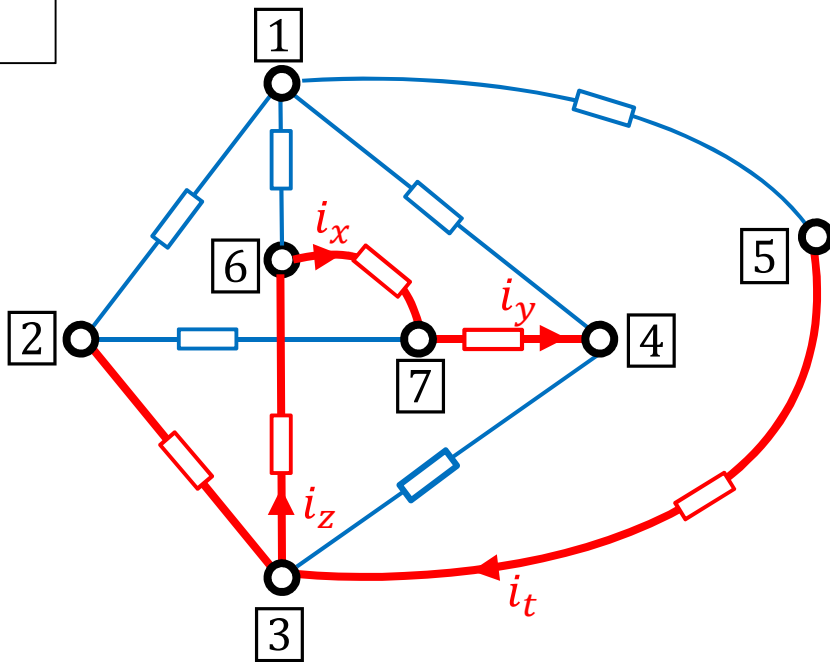

independent current variables

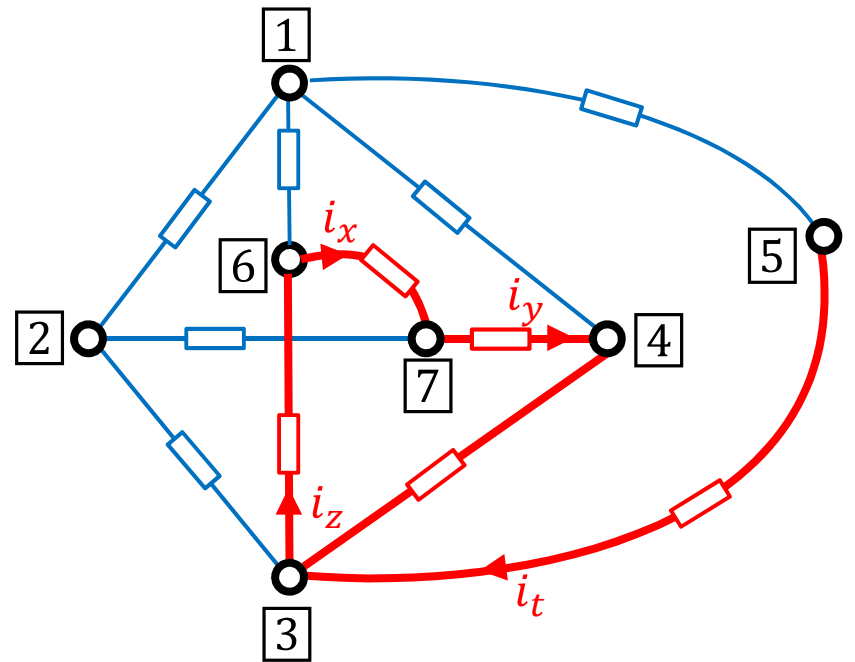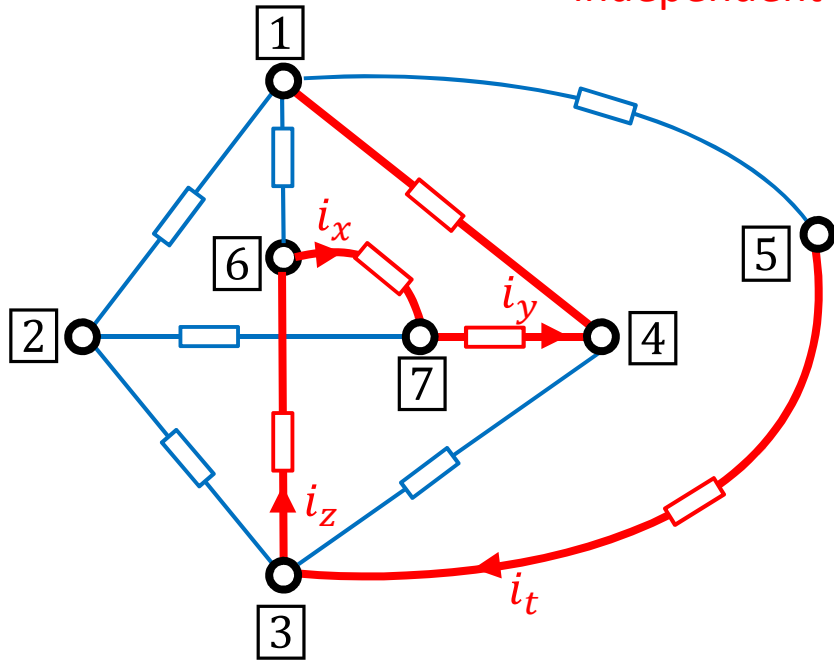

٢-الف

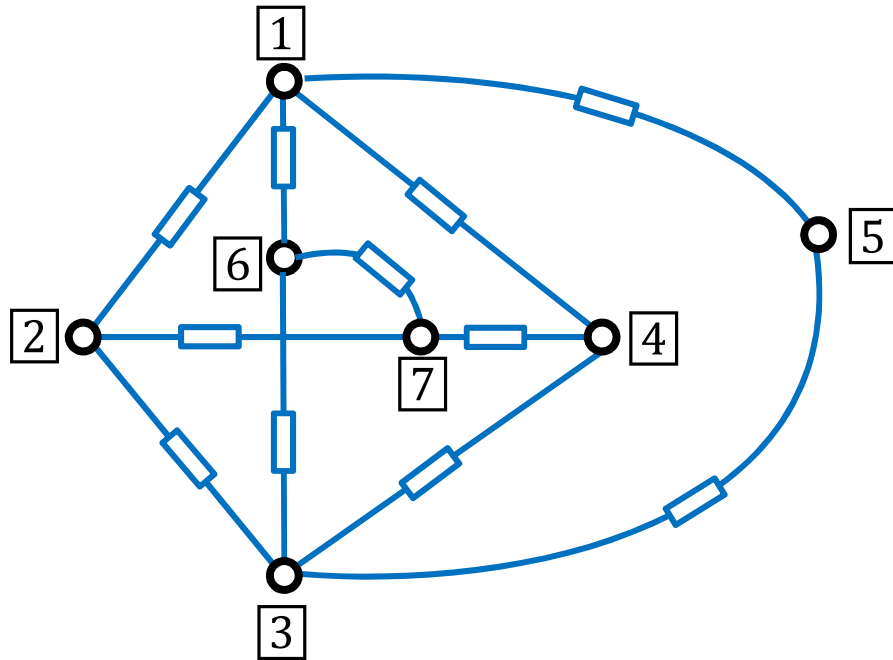

unknown currents & voltages = 22

independent KCL equations = 6


equations for each branch = 11



→ # of independent voltage equations = $22 - 11 - 6 = 5$

→ # of independent voltage variables = $11 - 5 = 6$

٢-ب

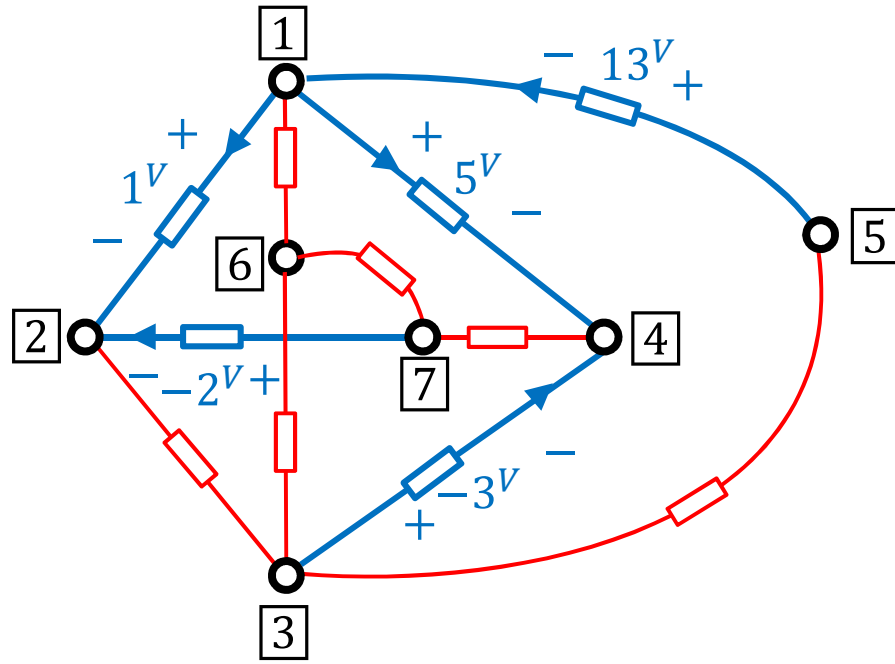

independent voltage variables = 6




given voltages = 5




→ unsolvable,
1 more indep. voltage is needed

۲-۱

independent voltage variables

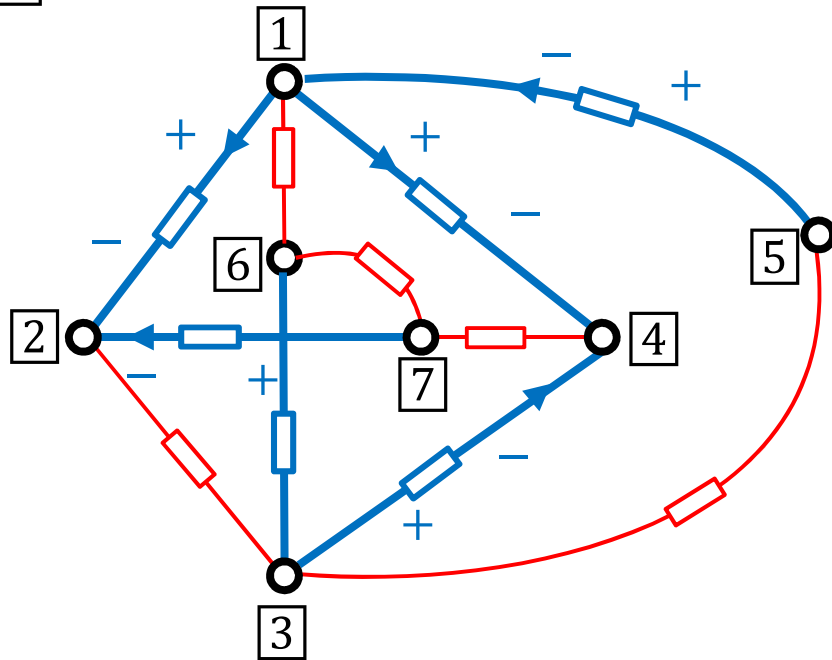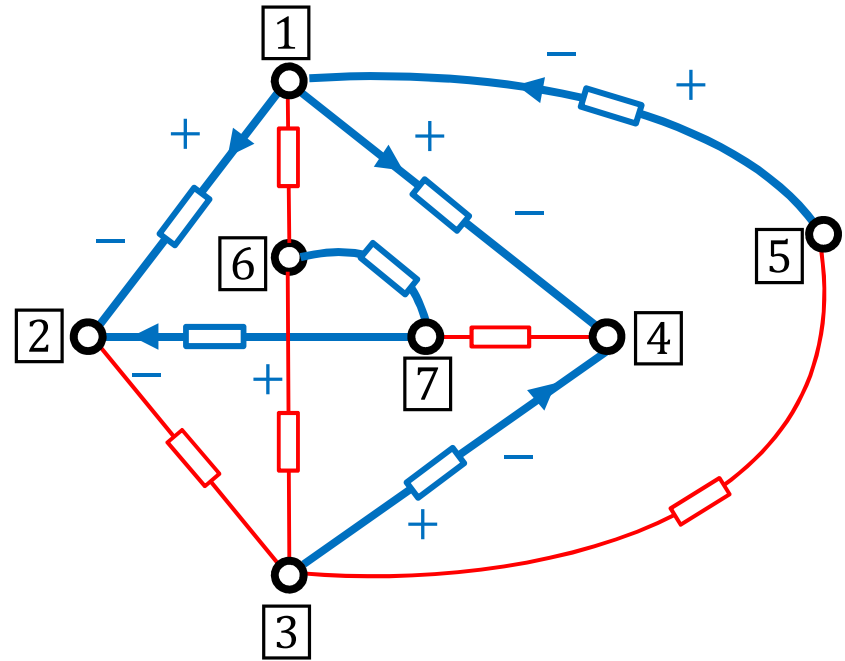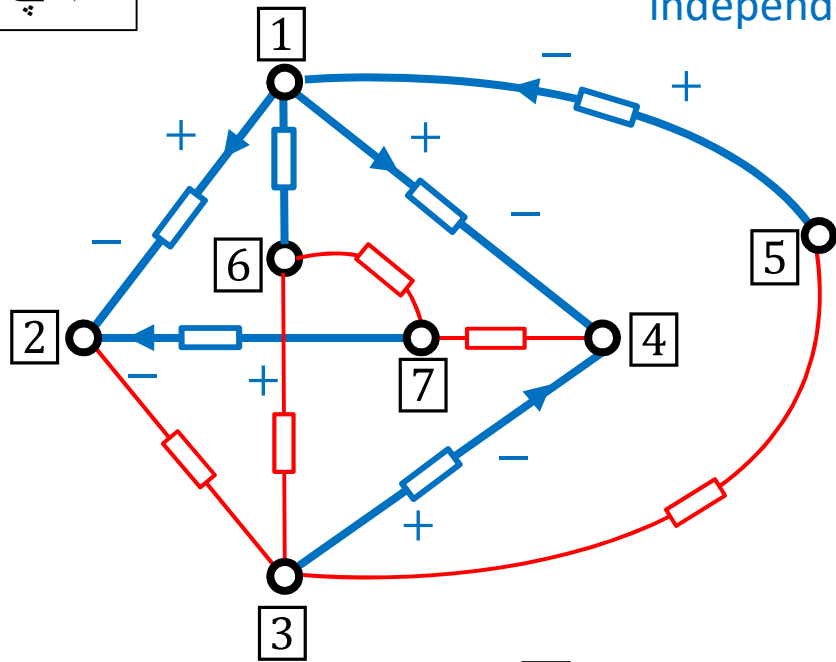

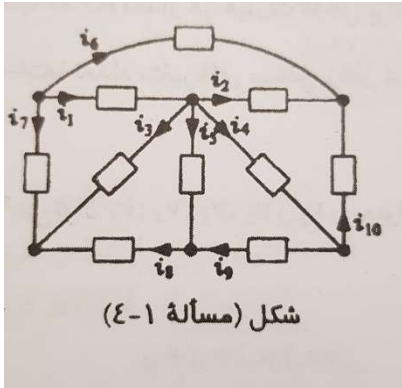

شکل (مسألة ۱-۴)

Subject.

Date.

سؤال ۴

الف

تعداد متغیر مستقل $i = 10 - 4 + 1 = 5$

① : $i_7 + i_4 + i_1 = 0$

② : $i_2 + i_3 + i_4 + i_5 - i_6 = 0$

③ : $-i_2 - i_4 - i_5 = 0$

④ : $-i_7 - i_3 - i_4 = 0$

⑤ : $-i_5 - i_7 + i_8 = 0$

کلی از حالتی که برخی جریان‌ها را بتوان مستقل گرفت i_1, i_2, i_3, i_4, i_5 مستقل باشند

با استفاده از $i_5 = i_1 - i_2 + i_3 - i_4$

روا خطی $i_7 = -i_1 - i_4$

باخت دیگر $i_8 = i_1 + i_4 - i_3$

جریان‌ها برابر $i_9 = i_4 + i_2 + i_3$

جریان‌ها مستقل $i_{10} = -i_2 - i_4$

$\sum v_i i_i = 0$

بصورت $(i_1, i_2, i_3, i_4, i_5)$ و (i_7, i_8, i_9, i_{10}) جایگزین

$\Rightarrow \sum v_i = 0$

با کت ب نیز می‌توانیم ثابت کنیم

$4 - 1 = 0$

تعداد متغیر مستقل

مستقل


v_1, v_2, v_3, v_4, v_5

کلی می‌توانیم ثابت کنیم

$\sum v_i = 0$

11

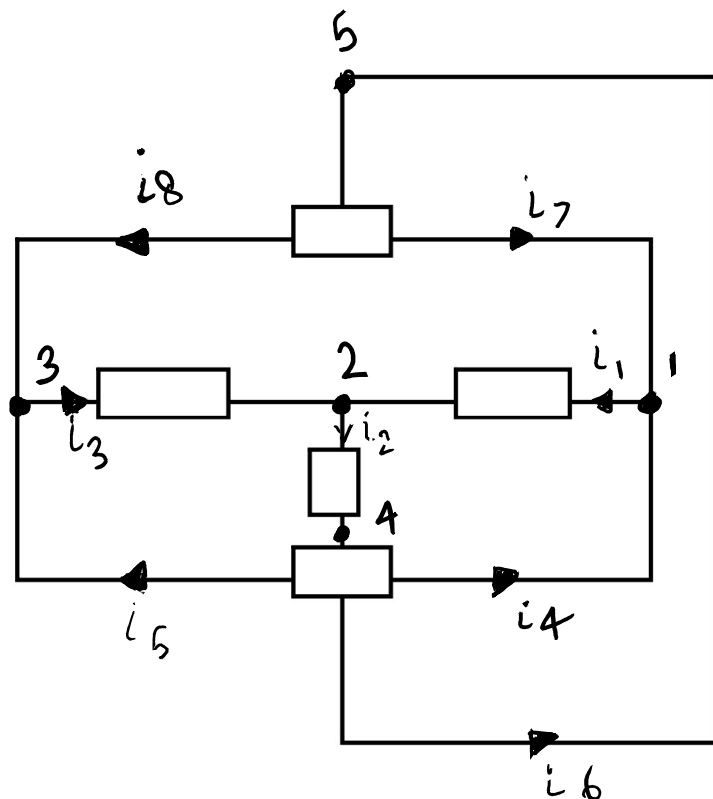نکته این مساله این است که برای مدار های دارای عناصر سه سر یا ۴ سر مانند مدار های شامل عناصر دو سر قوانین kvl و kcl برقرار است.



ککل:

$$1) \quad i_4 + i_7 = i_1$$


$$2) \quad i_1 + i_3 = i_2$$

$$3) \quad i_5 + i_8 = i_3$$

$$4) \quad i_4 + i_5 + i_6 = i_2$$

$$5) \quad i_7 + i_8 = i_6$$

11
/2

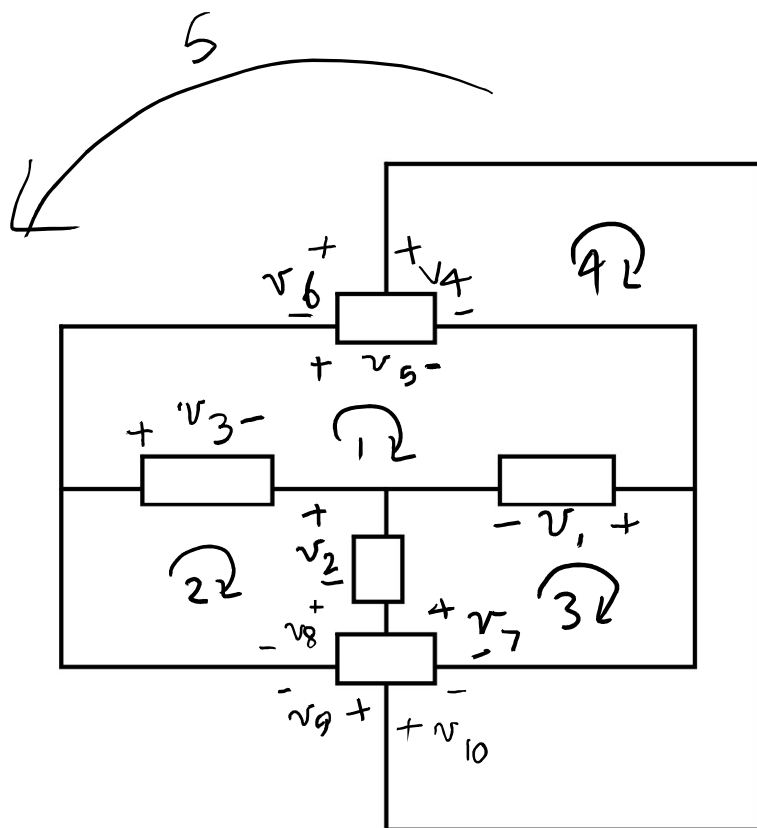

Loop KVL:

$$1) -v_3 + v_5 + v_1 = 0$$


$$2) v_3 + v_2 + v_8 = 0$$

$$3) -v_7 - v_2 - v_1 = 0$$

$$4) -v_4 + v_{10} = 0$$

$$5) -v_9 + v_6 = 0$$

14

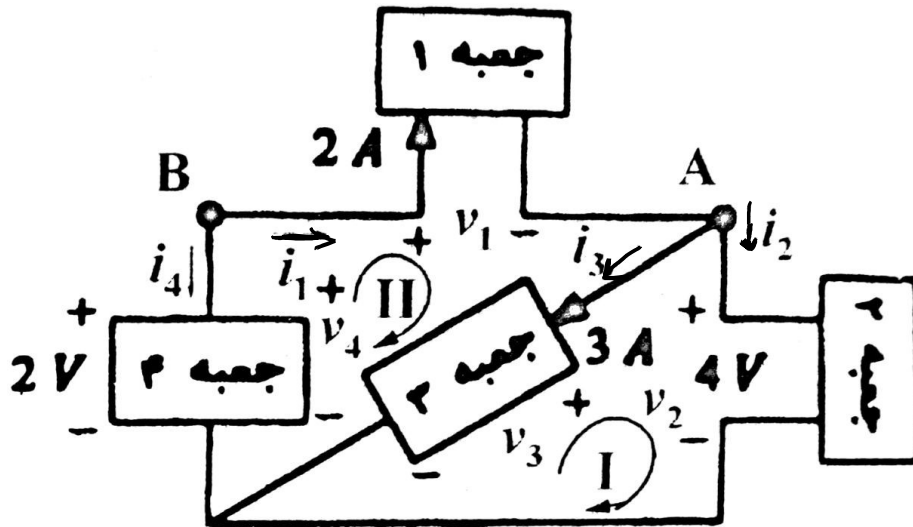

$$\text{KVL I) } v_2 - v_3 = 0 \Rightarrow \boxed{v_3 = 4V}$$

$$\text{KVL II) } v_1 + v_3 - v_4 = 0 \Rightarrow$$

$$\boxed{v_1 = 2 - 4 = -2V}$$

$$\text{KCL A) } i_1 = i_2 + i_3 \Rightarrow \boxed{i_2 = -1A}$$

$$\text{KCL B) } -i_1 = i_4 \Rightarrow \boxed{i_4 = -2A}$$

$$P = v i \Rightarrow \begin{cases} P_1 = -2 \times 2 = -4 \text{ W} \\ P_2 = 4 \times -1 = -4 \text{ W} \\ P_3 = 4 \times 3 = 12 \text{ W} \\ P_4 = 2 \times -2 = -4 \text{ W} \end{cases}$$

$$\sum_{i=1}^4 P_i = -4 - 4 + 12 - 4 = 0$$

صورتی از قضیه تلن برقرار است