
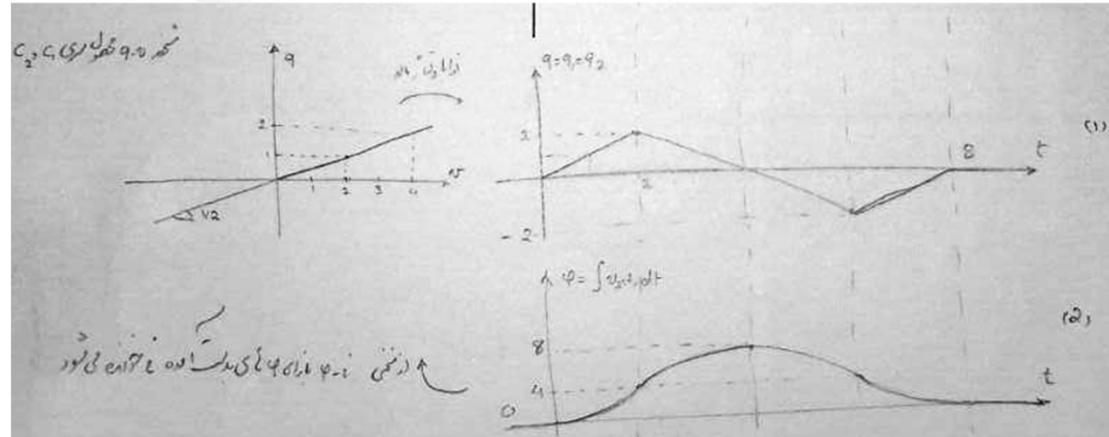



Part B

1.




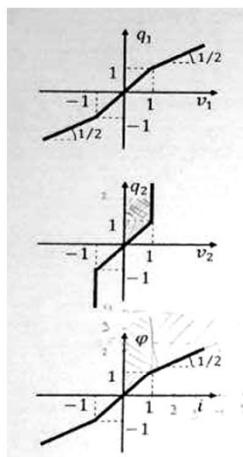


$$\mathcal{E}_M(t=2) = \frac{1}{2} + 4 + \frac{3 \times 6}{2} = 13.5$$
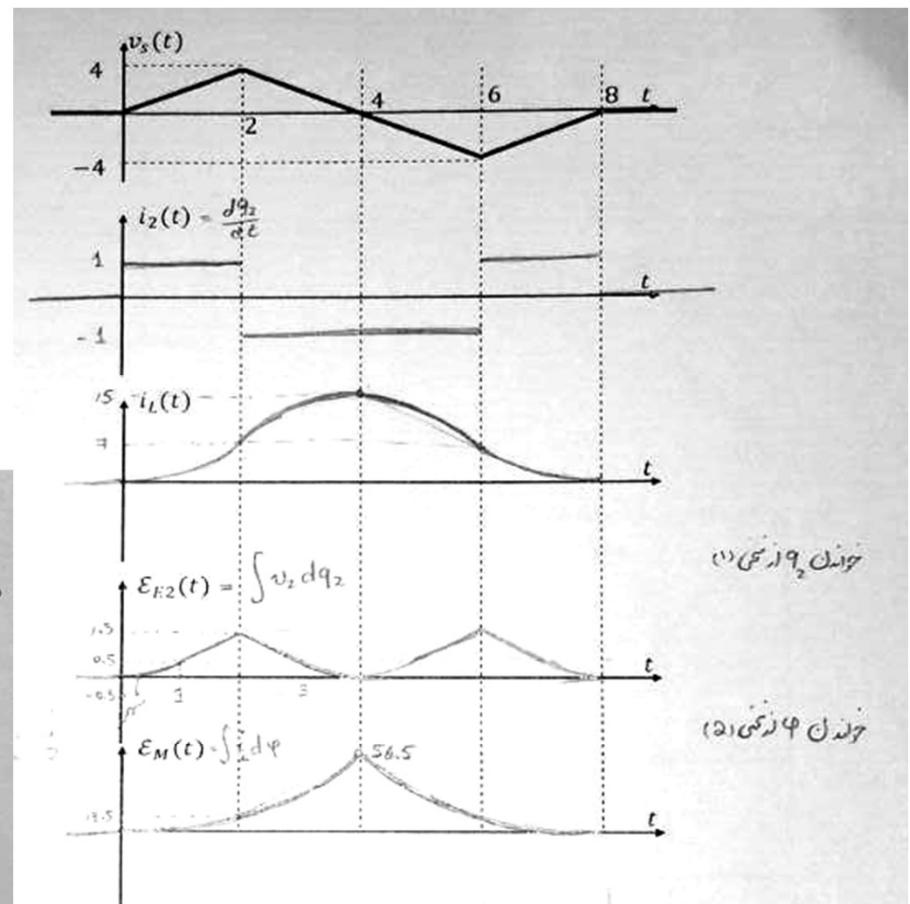
$$\mathcal{E}_M(t=4) = \frac{1}{2} + 7 + \frac{7 \times 19}{2} = 56.5$$




2

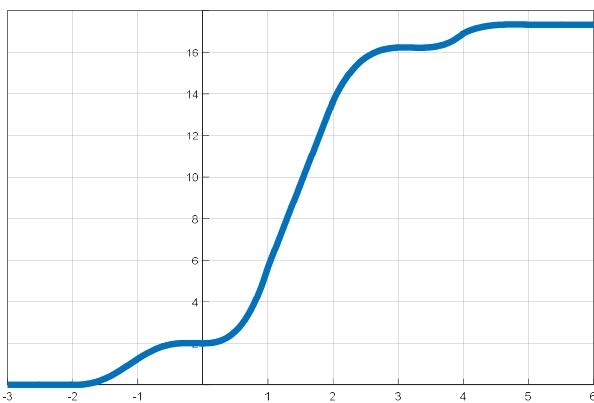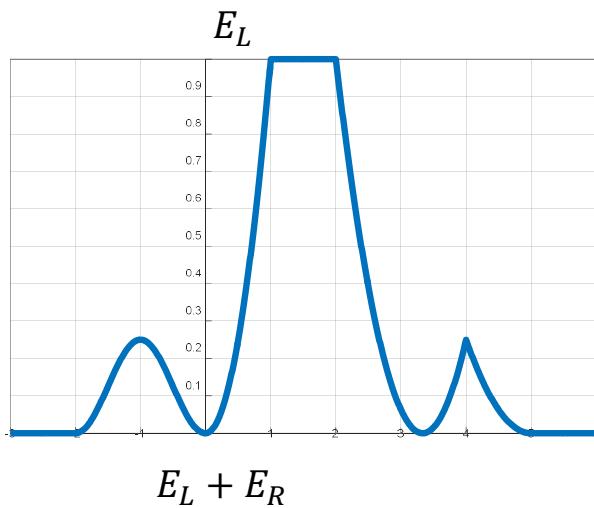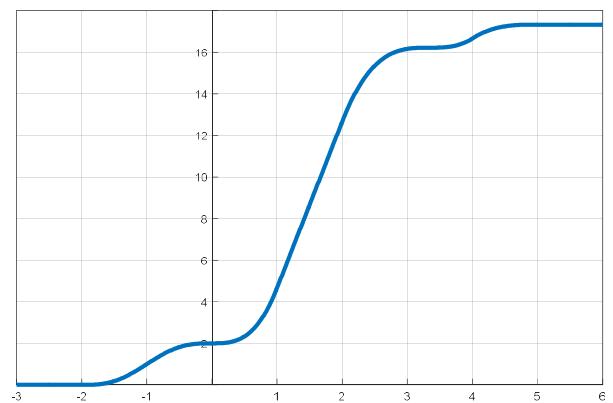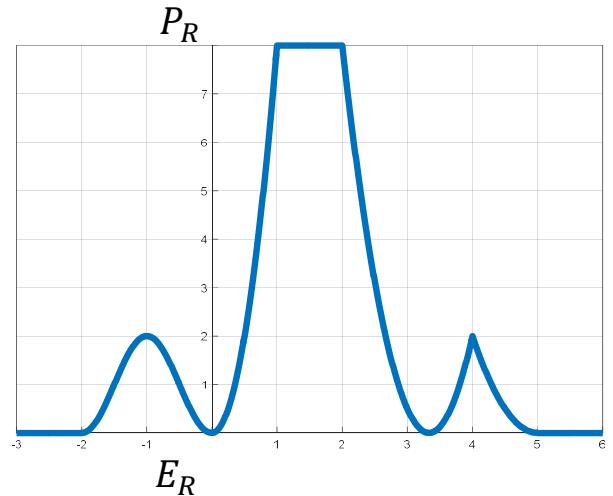


مثابه مساله ۶ قسمت الف

J16


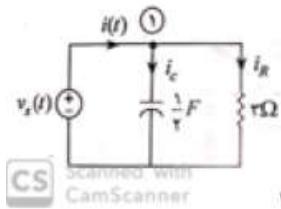


$$\begin{aligned} KCL: i(t) &= i_R + i_c \\ i_c &= c \frac{dv_s}{dt} \\ i_R &= \frac{v_s}{R} \end{aligned}$$
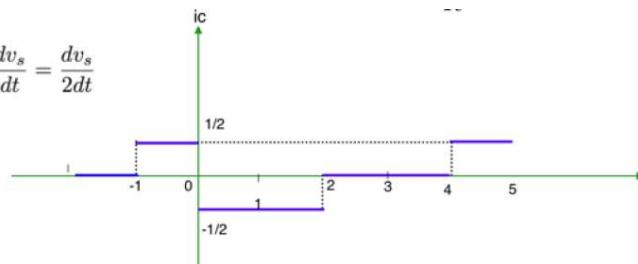
$$i_c = c \frac{dv_s}{dt} = \frac{dv_s}{2dt}$$




$$i_R = \frac{v_s}{R} = \frac{v_s}{3}$$

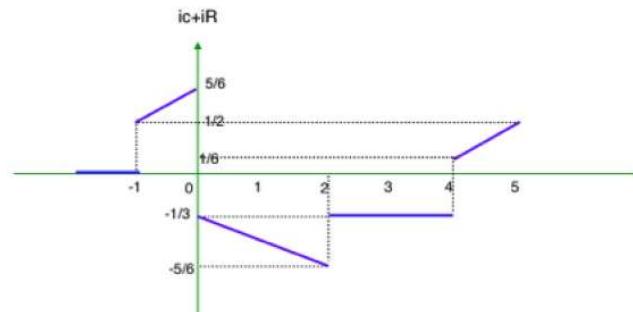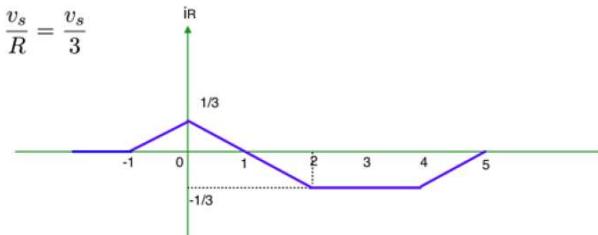

ج) خازنی با $C = \frac{1}{F}$ و $v_c(t) = 0$ دو سر منبع x وصل شده است.

الف) اگر منبع از نوع ولتاژ باشد، شکل موج جریان گذارنده از خازن را درس کنید.

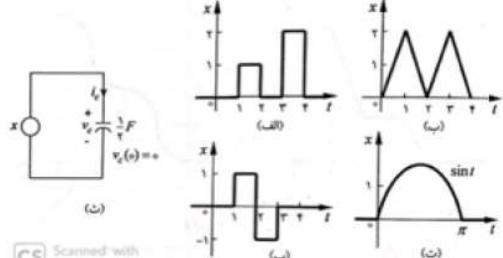
ب) اگر منبع از نوع جریان باشد، شکل موج ولتاژ در سر خازن را درس کنید.



Scanned with

الف
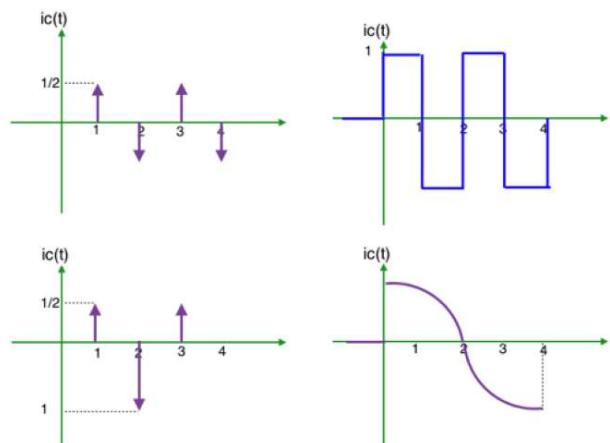
$$i_c = C \frac{dv_c}{dt} = \frac{dv_c}{2dt}$$



$$i_c = C \frac{dv_c}{dt} \rightarrow +i_c + v_c \text{ از اینجا از انتگرال می‌بریم } \rightarrow \int_{t_0}^t i_c dt = \int_{t_0}^t C \frac{dv_c}{dt} dt = C(v(t) - v(t_0))$$

$$\Rightarrow v(t) = \frac{1}{C} \int_{t_0}^t i_c(t) + v(t_0)$$

الف) $v(1) = 0$ (جواب تین برابر است)
برای $1 < t < 2 \rightarrow v(t) = 2 \int_1^t 1 dt + 0 = 2(t-1)$

$v(2) = 2$ \rightarrow برای $2 < t < 3 \rightarrow v(t) = 2 \times 0 + v(2) = 2$


$v(3) = 2$ \rightarrow برای $3 < t < 4 \rightarrow v(t) = 2 \int_3^t 2 dt + 2 = 4(t-3) + 2 = 4t - 10$



ب) $v(0) = 0 \rightarrow$ برای $0 < t < 1 \rightarrow v(t) = 2 \int_0^t 2t dt + 0 = 2t^2$

$i_c(t) = 2t$ $v(1) = 2 \rightarrow$ برای $1 < t < 2 \rightarrow v(t) = 2 \int_1^t 2(t-1) dt + 2 = 2(t(t-1) - t^2 + 1) + 2 = 2t^2 - 2t + 2$

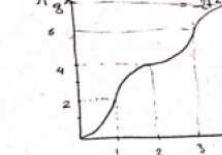$v(2) = 4 \rightarrow$ وضایعی احتمالی می‌شوند




ج) $v(1) = 0 \rightarrow$ برای $1 < t < 2 \rightarrow v(t) = 2 \int_1^t 1 dt + 0 = 2(t-1)$








$v(2) = 2 \rightarrow$ برای $2 < t < 3 \rightarrow v(t) = 2 \int_2^t 1 dt + 2 = 2(t-2) + 2 = 2t - 2$



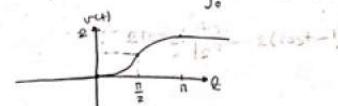د) $v(0) = 0 \rightarrow$ برای $0 < t < \pi \rightarrow v(t) = 2 \int_0^t \sin t dt + 0 = 2(-\cos t)$




J25

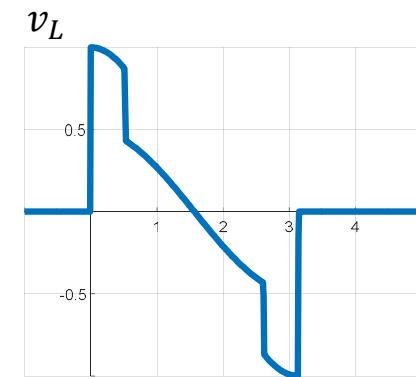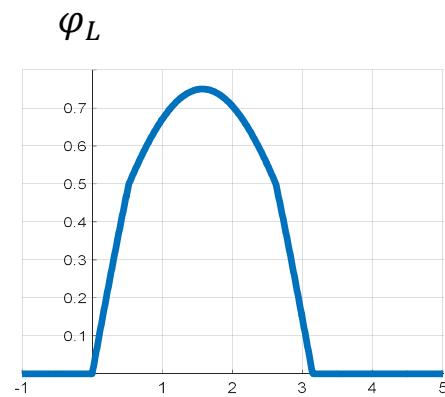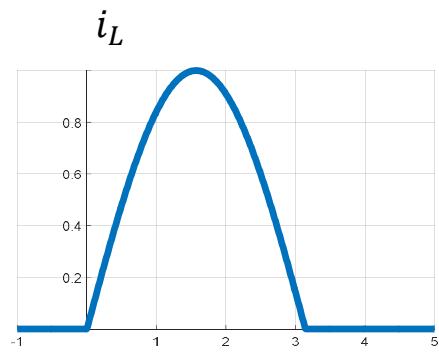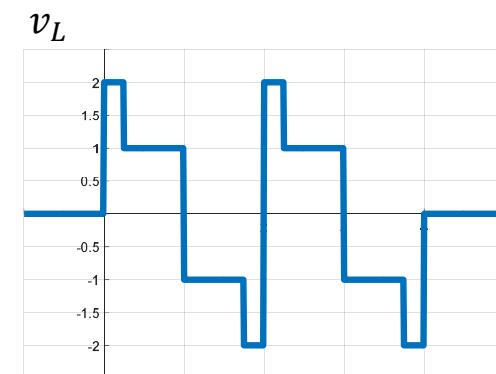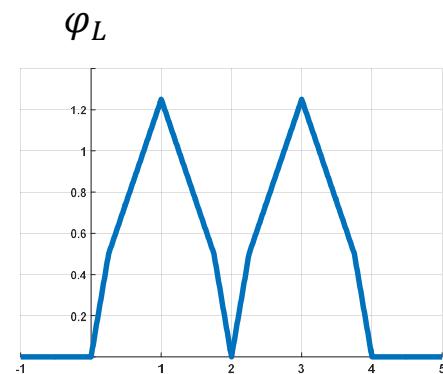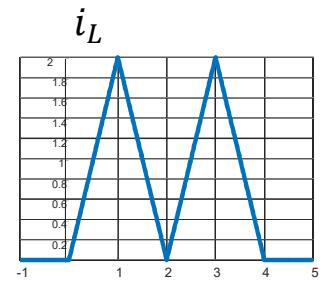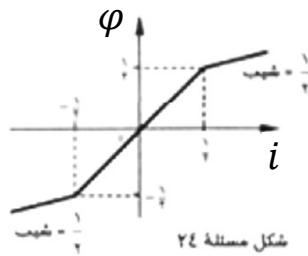


J27


$$i(t) = 10te^{-5t}u(t)$$

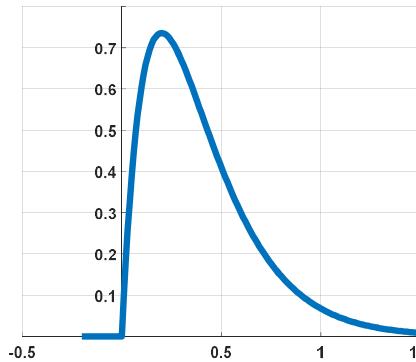

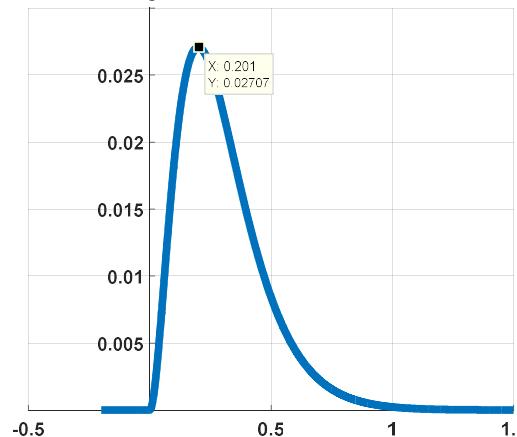
$$w(t) = \int p(t)dt = 5t^2e^{-10t}u(t)$$


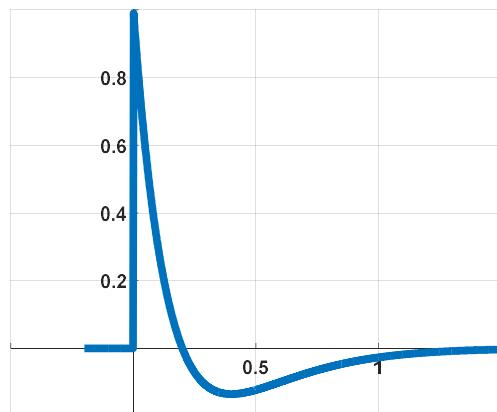
$$v_L(t) = 0.1 \frac{di_l}{dt} = (1 - 5t)e^{-5t}u(t)$$


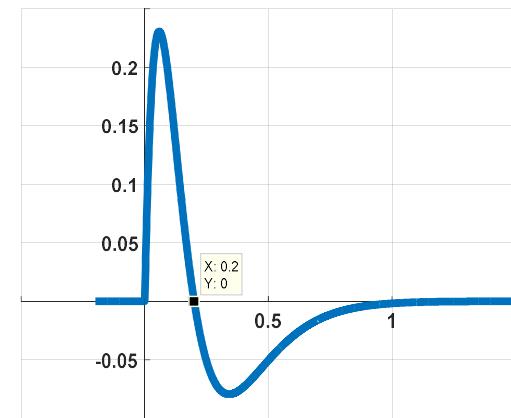
$$p(t) = v(t)i(t) = (10 - 50t)te^{-10t}u(t)$$



$t < 0.2$: Energy stores

$t > 0.2$: Energy receives

$$p(t = .2) = 0 \rightarrow$$

$$w_{max} = w(0.2) = 0.027 J$$